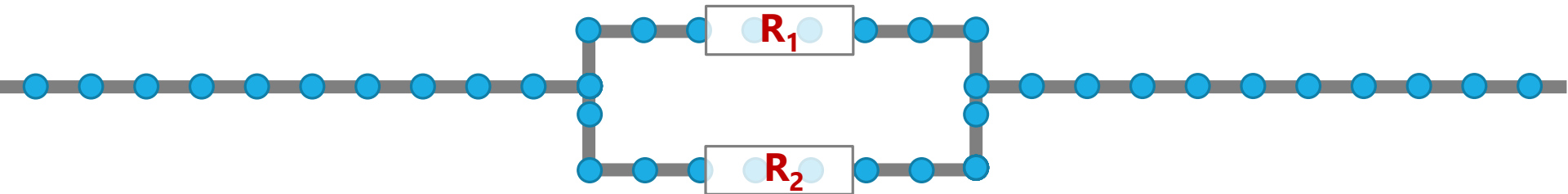


# Equivalent Resistance

---

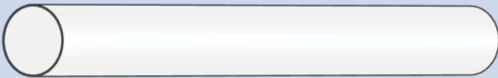

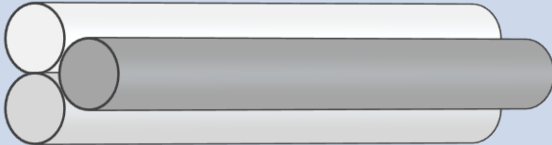
IB PHYSICS | ELECTRICITY

# Series and Parallel



# Straw “Resistor”

A good physical model for current travelling through resistors is blowing through a straw.



<b>1 resistor</b>	
<b>3 resistors in series</b>	
<b>3 resistors in parallel</b>	

# Combining Resistors


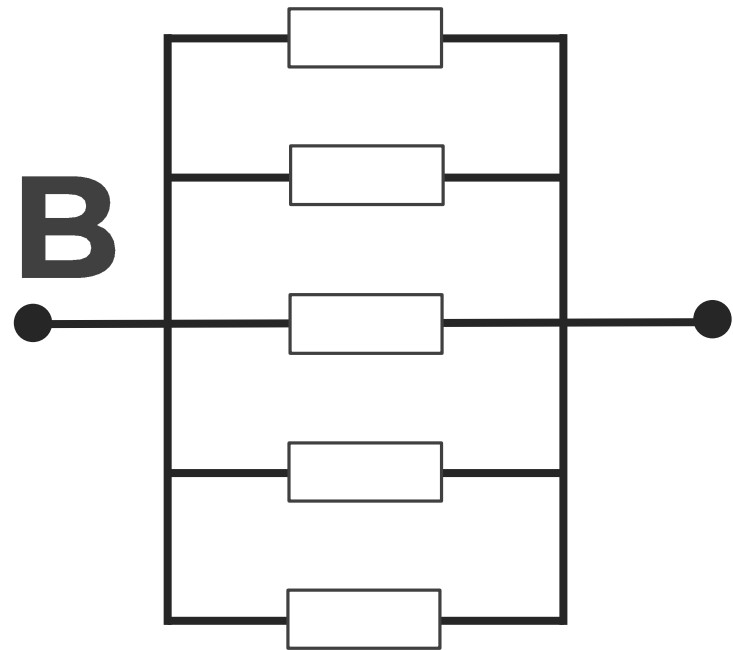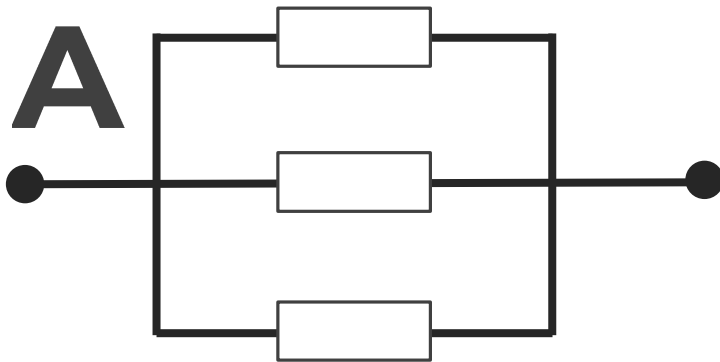
# Compare these Combos...


Which example has the lowest overall resistance?  
Assume that every resistor is the same.



# Combining Resistors | Series

When combining resistors in series, the resistances are simply added up as if they were one large resistor



$$R_{total} = R_1 + R_2 + \dots$$

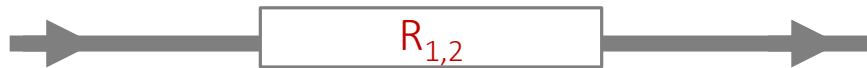


# Combining Resistors | Parallel

When combining resistors in parallel, the overall resistance decreases to produce a smaller equivalent resistance
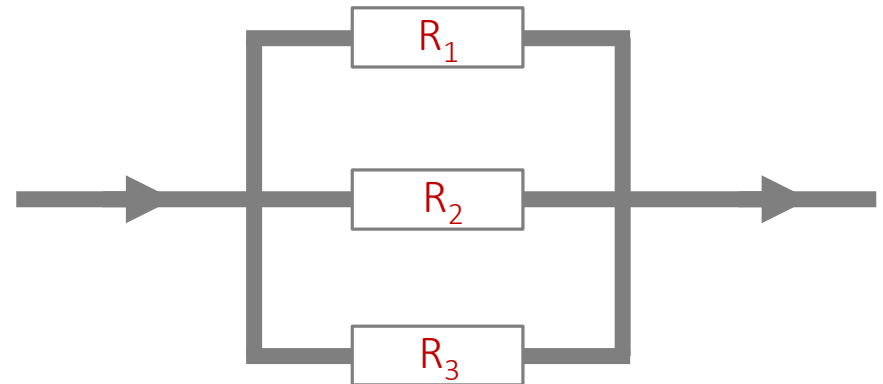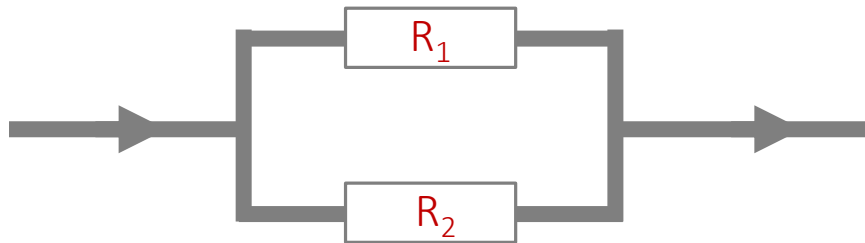
$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$



# Combining Resistors – Try This

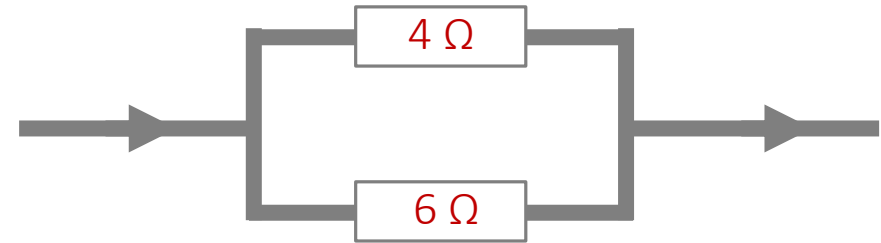



# IB Physics Data Booklet

## Sub-topic 5.1 – Electric fields

$$I = \frac{\Delta q}{\Delta t}$$

$$F = k \frac{q_1 q_2}{r^2}$$

$$k = \frac{1}{4\pi\epsilon_0}$$

$$V = \frac{W}{q}$$

$$E = \frac{F}{q}$$

$$I = nAvq$$

## Sub-topic 5.2 – Heating effect of electric currents

Kirchhoff's circuit laws:

$$\Sigma V = 0 \text{ (loop)}$$

$$\Sigma I = 0 \text{ (junction)}$$

$$R = \frac{V}{I}$$

$$P = VI = I^2 R = \frac{V^2}{R}$$

$$R_{\text{total}} = R_1 + R_2 + \dots$$

$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$\rho = \frac{RA}{L}$$

## Sub-topic 5.3 – Electric cells


$$\mathcal{E} = I(R + r)$$

## Sub-topic 5.4 – Magnetic effects of electric currents


$$F = qvB \sin \theta$$

$$F = BIL \sin \theta$$


# Equivalent Resistance

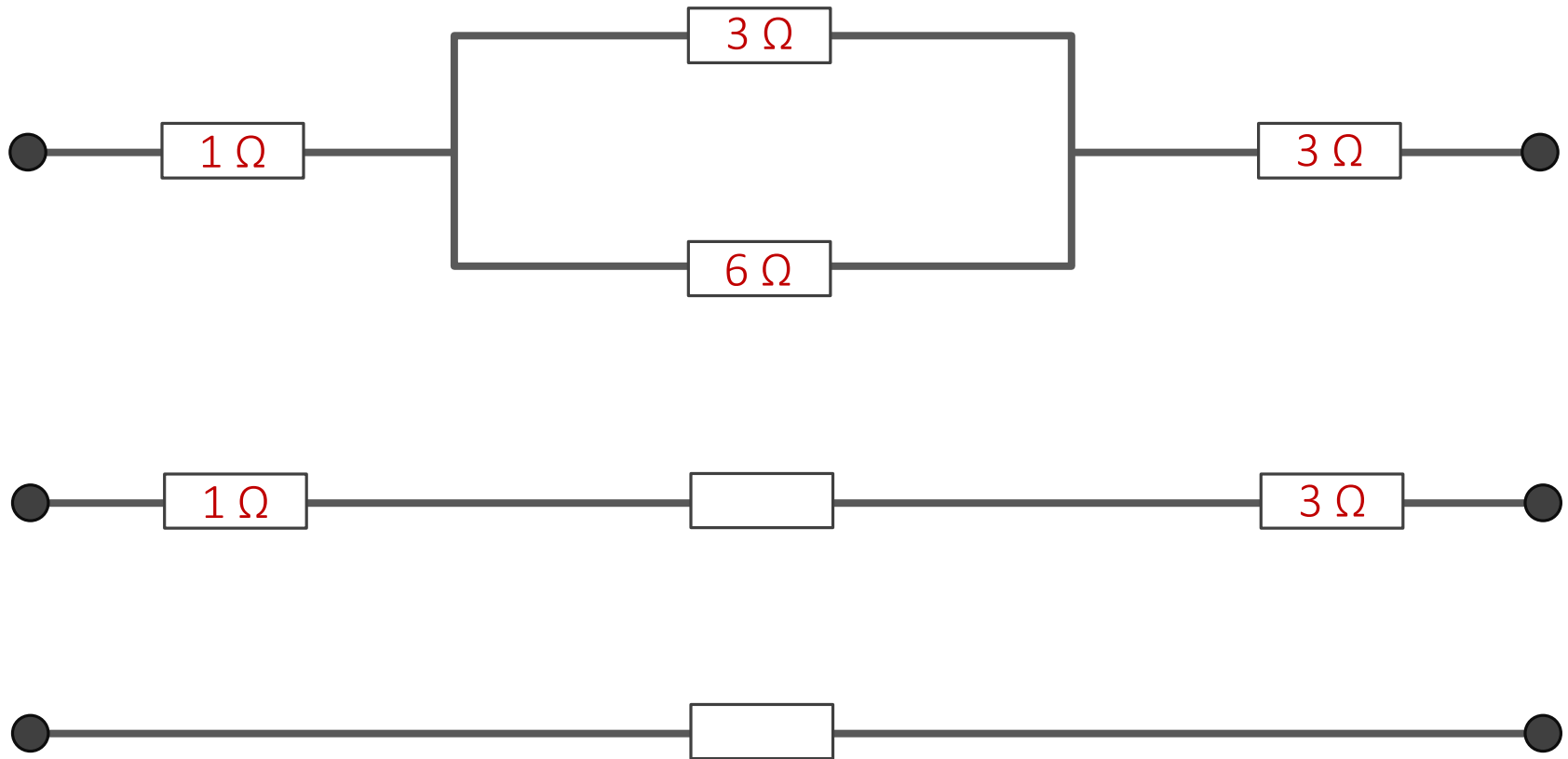

# Try This | Equivalent Resistance

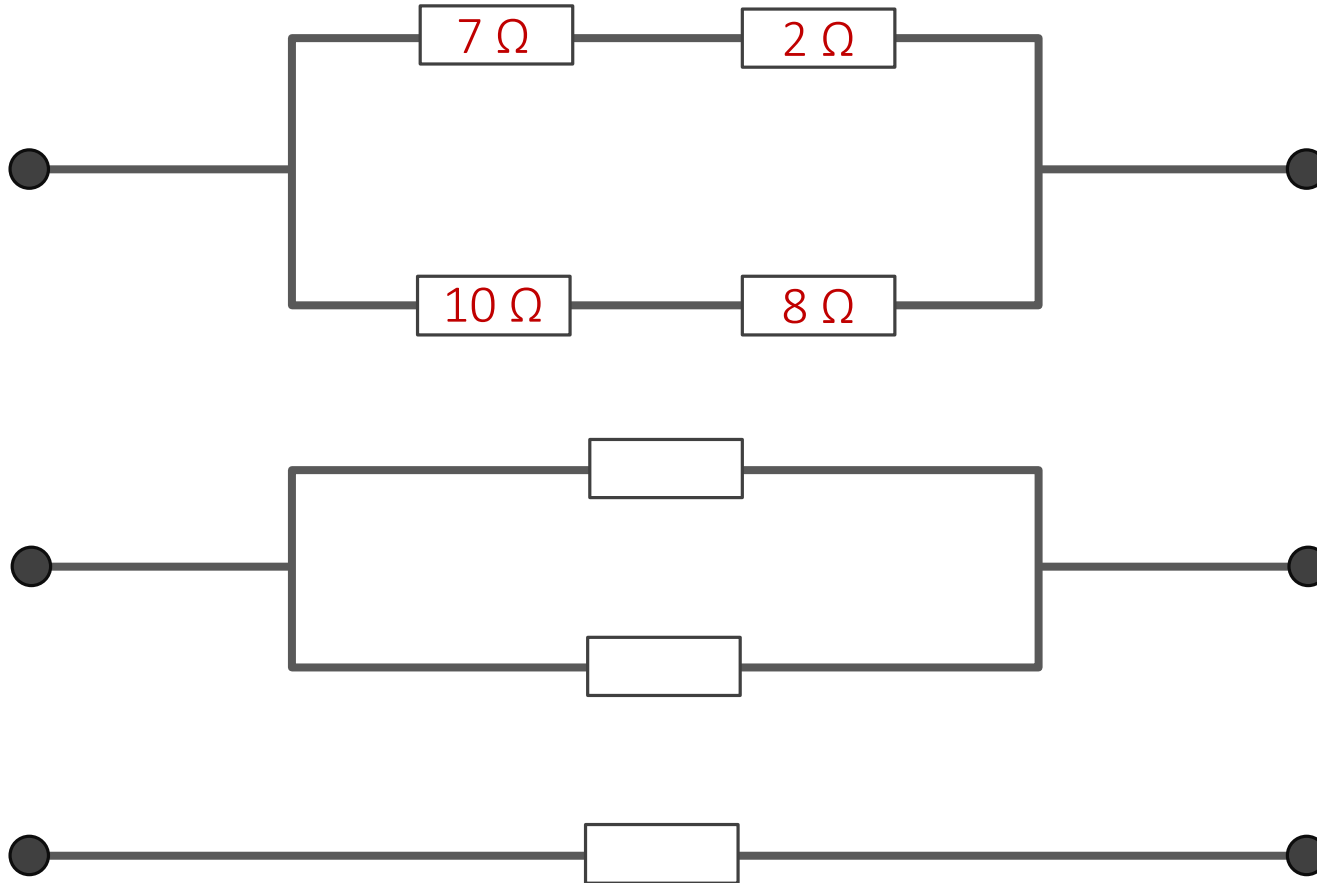

# This could be bigger...

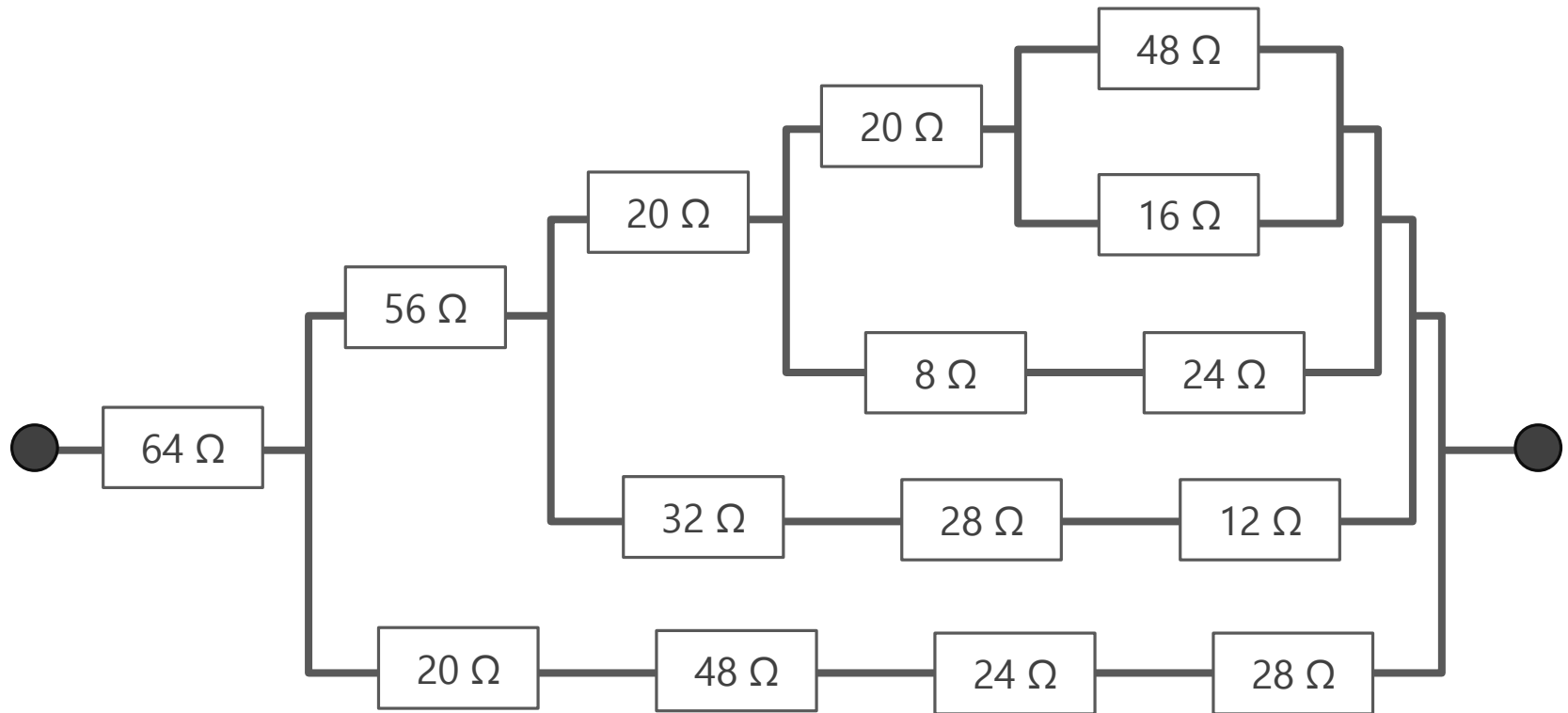

# Lesson Takeaways

- ❑ I can calculate the equivalent resistance for combinations of resistors in series and parallel
- ❑ I can systematically step through the calculation of the equivalent resistance for a complex combination