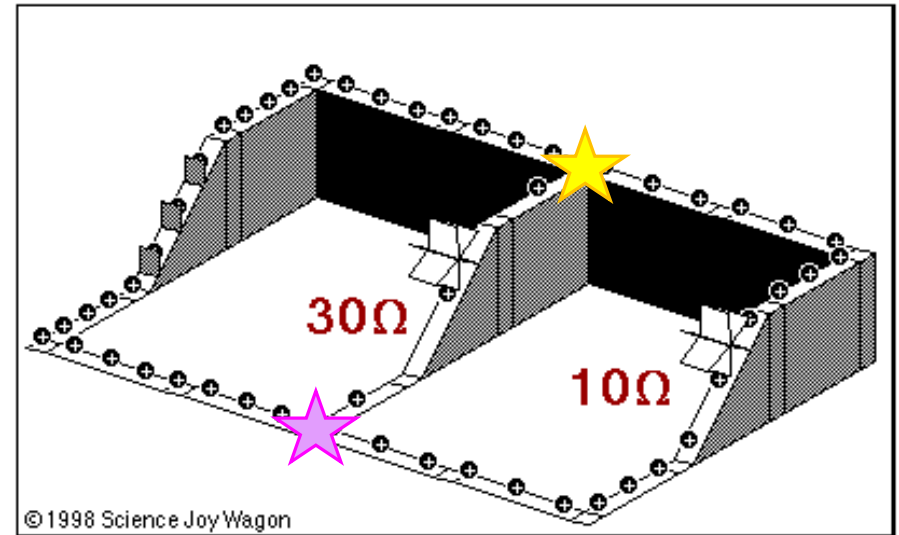


Circuit Analysis


IB PHYSICS | ELECTRICITY

Review of Parallel Circuits


- Separate branches
- Current splits up between the different pathways





★ Junctions ★

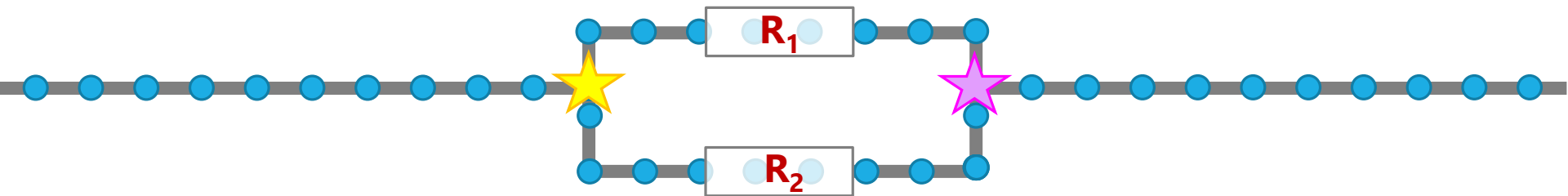


Kirchhoff's First Law

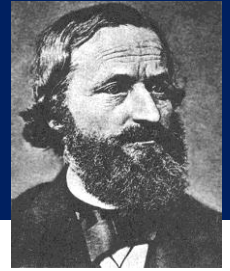

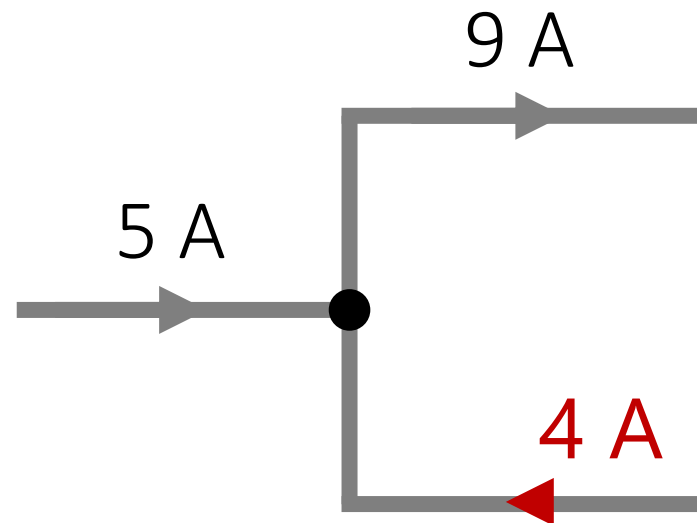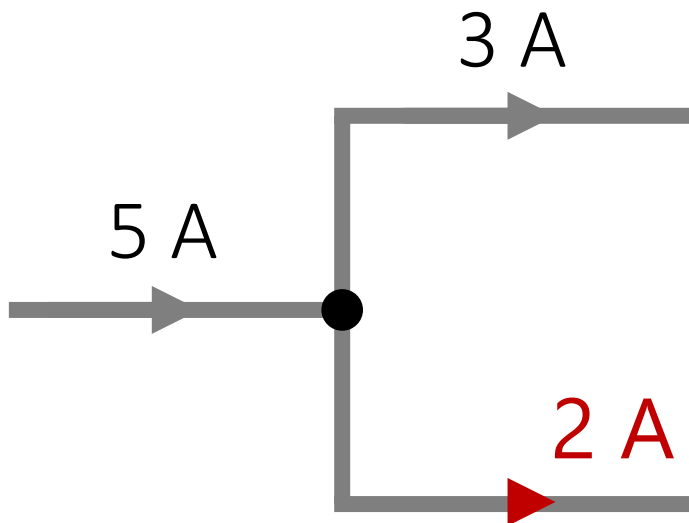The total current coming into a junction must equal the total current leaving the same junction





Kirchhoff's First Law

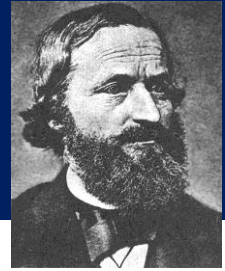

$$\Sigma I = 0 \text{ (junction)}$$

Entering Junction	$\rightarrow \bullet$	Positive
Exiting Junction	$\bullet \rightarrow$	Negative

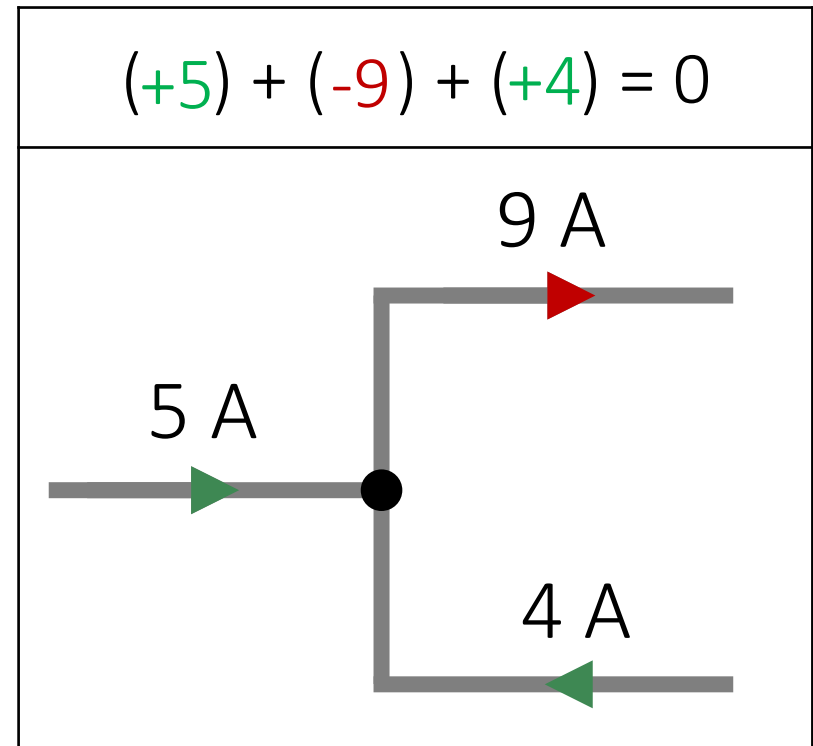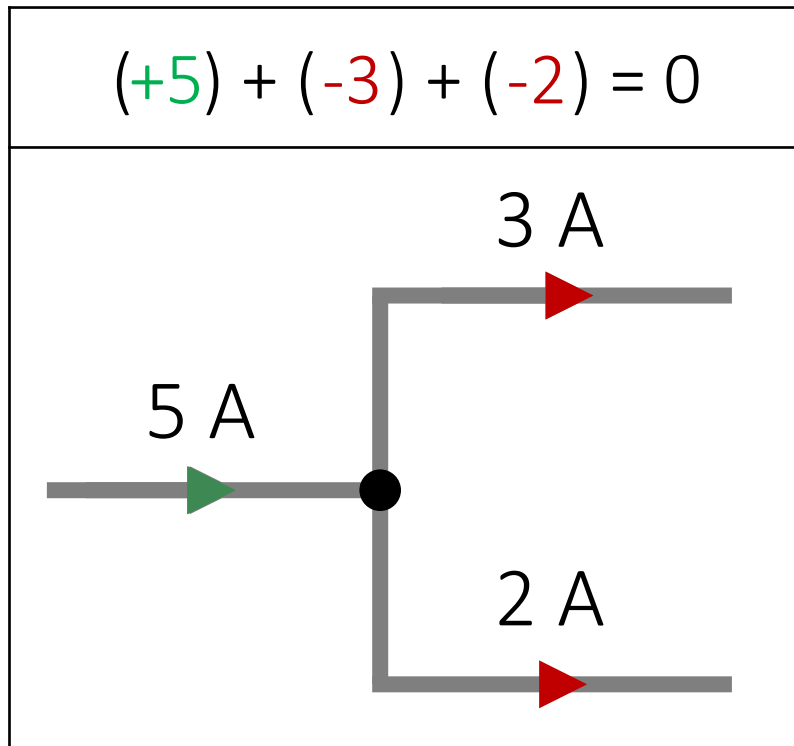

IB Physics Data Booklet

Sub-topic 5.1 – Electric fields

$$I = \frac{\Delta q}{\Delta t}$$

$$F = k \frac{q_1 q_2}{r^2}$$

$$k = \frac{1}{4\pi\epsilon_0}$$

$$V = \frac{W}{q}$$

$$E = \frac{F}{q}$$

$$I = nAvq$$

Sub-topic 5.2 – Heating effect of electric currents

Kirchhoff's circuit laws:

$$\Sigma V = 0 \text{ (loop)}$$

$$\Sigma I = 0 \text{ (junction)}$$

$$R = \frac{V}{I}$$

$$P = VI = I^2 R = \frac{V^2}{R}$$

$$R_{\text{total}} = R_1 + R_2 + \dots$$

$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$\rho = \frac{RA}{L}$$

Sub-topic 5.3 – Electric cells


$$\mathcal{E} = I(R + r)$$

Sub-topic 5.4 – Magnetic effects of electric currents


$$F = qvB \sin \theta$$

$$F = BIL \sin \theta$$


Find the Missing Currents

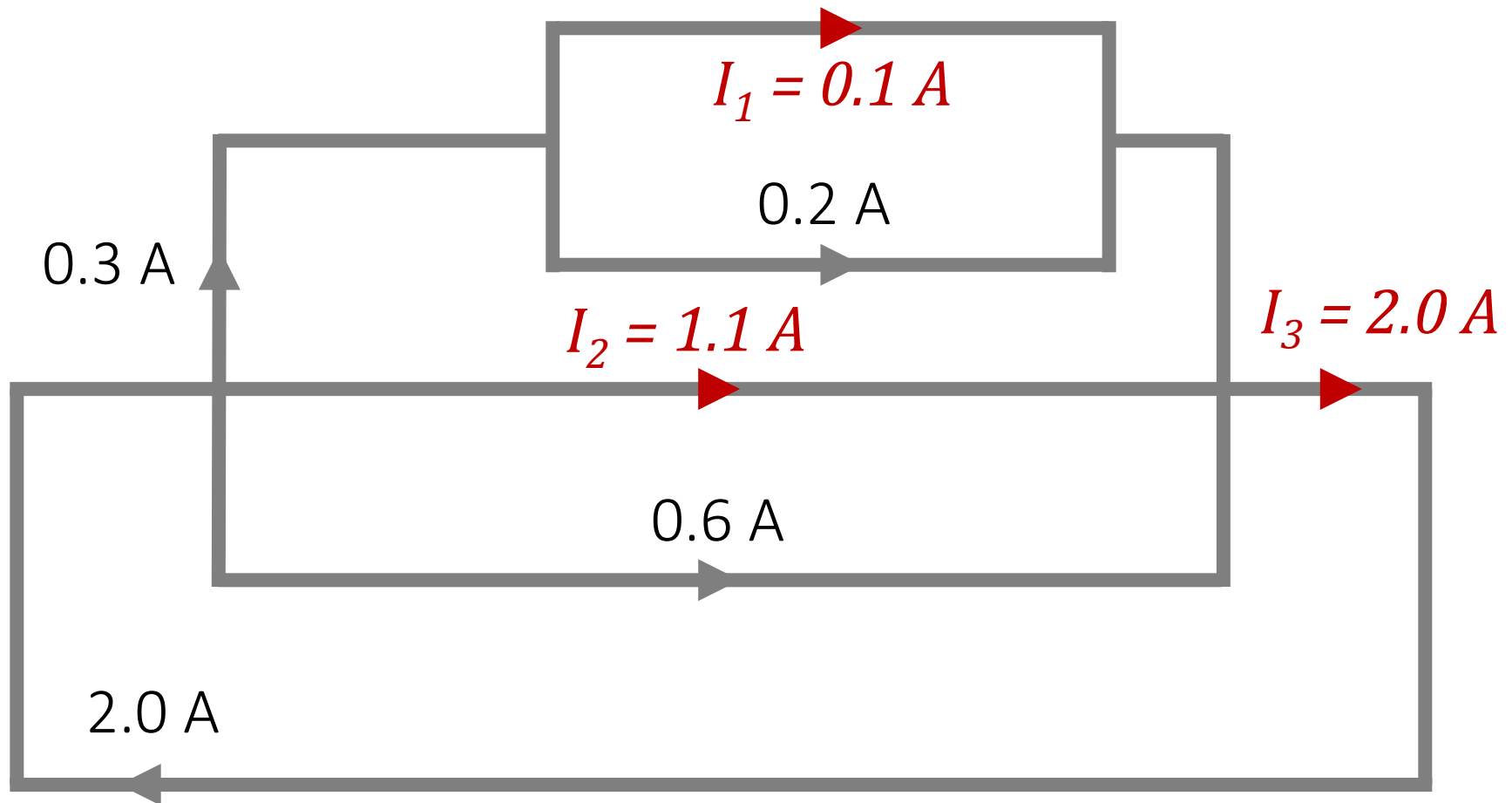

Follow the Current...

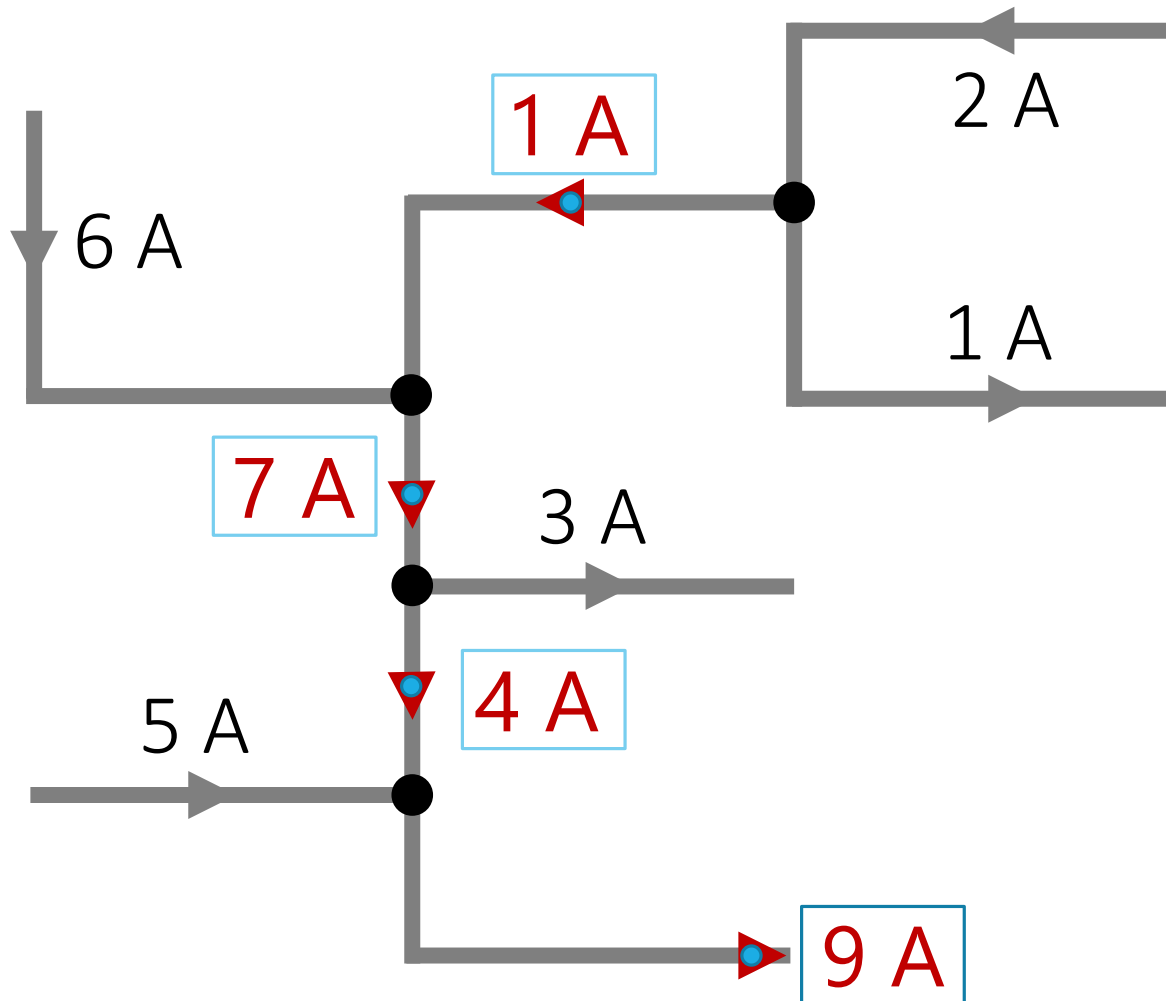


Review of the Water Flow Model

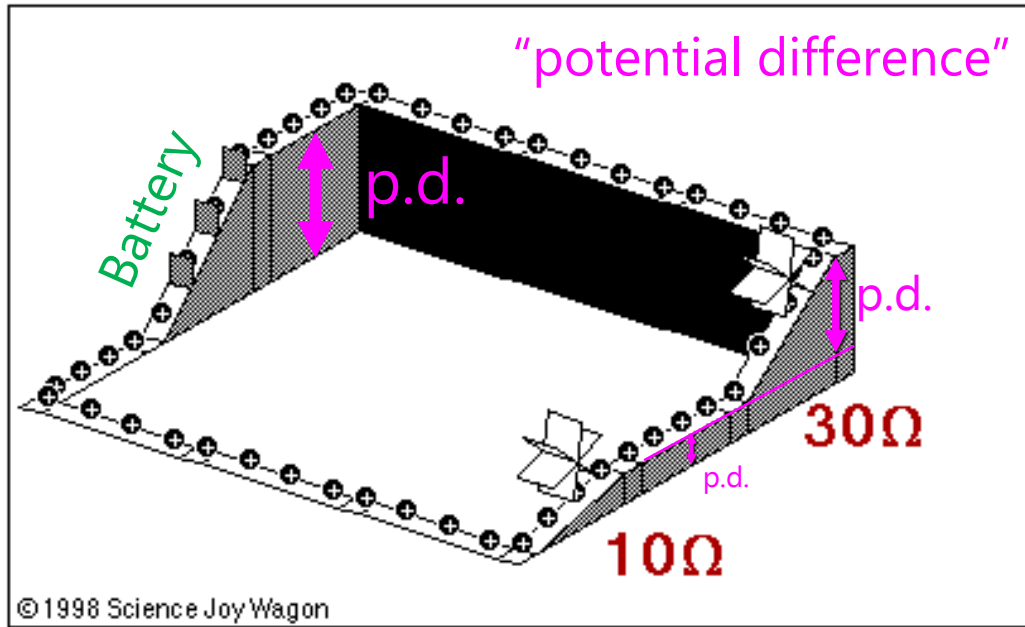


The voltage used by the resistors equals the voltage supplied by the battery

Each resistor has a "voltage drop"

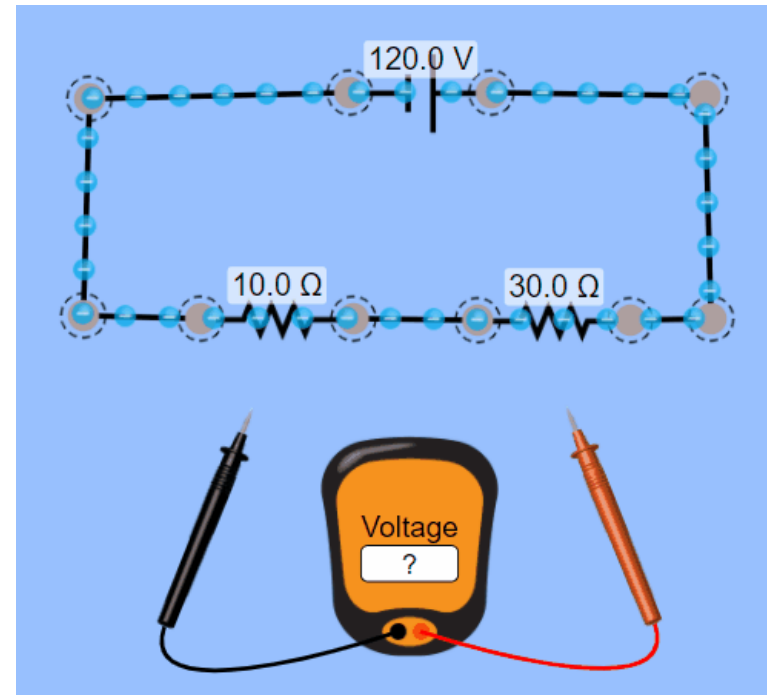

Kirchhoff's Second Law

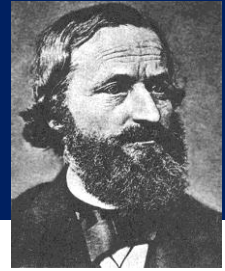

The sum of the voltages (potential differences) provided must equal the voltages dissipated across components


$$\Sigma V = 0 \text{ (loop)}$$

Across Batteries

Negative to Positive	$\rightarrow \text{+}$	Positive
Positive to Negative	$\rightarrow \text{ }$	Negative

Over Resistors:


Always Negative

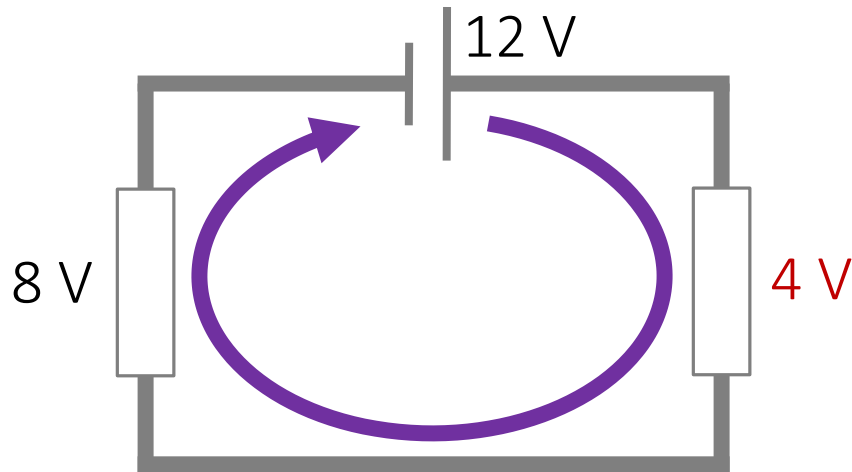

$$(+12) + (-4) + (-8) = 0$$

Resistor

Kirchhoff's Second Law

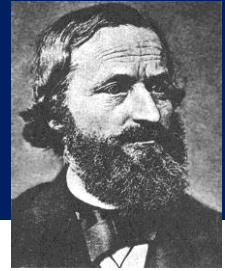

$$\Sigma V = 0 \text{ (loop)}$$

Across Batteries


Negative to Positive	$\rightarrow \text{+} \text{---} \text{+}$	Positive
Positive to Negative	$\rightarrow \text{---} \text{+}$	Negative

Over Resistors:

Always Negative

$$(+12) + (-2) + (-9) + (-1) = 0$$

Resistor

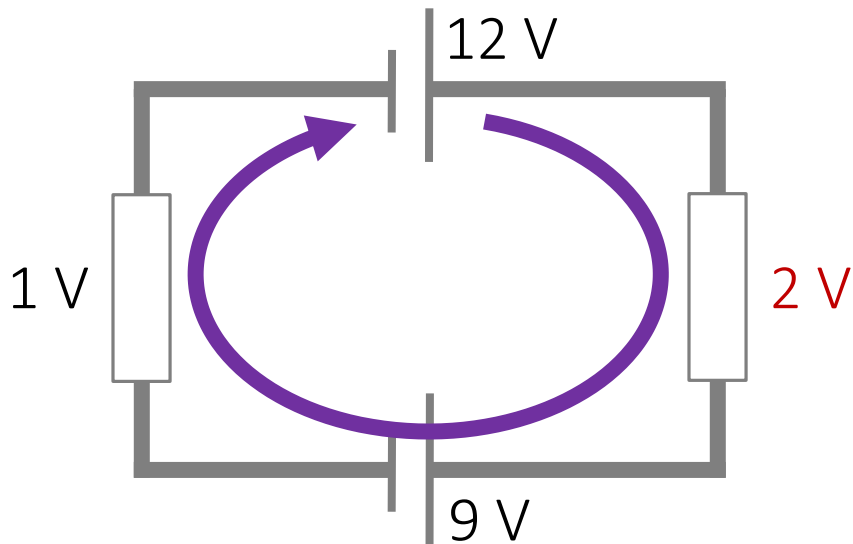

IB Physics Data Booklet

Sub-topic 5.1 – Electric fields

$$I = \frac{\Delta q}{\Delta t}$$

$$F = k \frac{q_1 q_2}{r^2}$$

$$k = \frac{1}{4\pi\epsilon_0}$$

$$V = \frac{W}{q}$$

$$E = \frac{F}{q}$$

$$I = nAvq$$

Sub-topic 5.2 – Heating effect of electric currents

Kirchhoff's circuit laws:

$$\Sigma V = 0 \text{ (loop)}$$

$$\Sigma I = 0 \text{ (junction)}$$

$$R = \frac{V}{I}$$

$$P = VI = I^2 R = \frac{V^2}{R}$$

$$R_{\text{total}} = R_1 + R_2 + \dots$$

$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$\rho = \frac{RA}{L}$$

Sub-topic 5.3 – Electric cells

$$\mathcal{E} = I(R + r)$$

Sub-topic 5.4 – Magnetic effects of electric currents

$$F = qvB \sin \theta$$

$$F = BIL \sin \theta$$

The Tools for your Toolbox ☺

Ohm's Law: If you know two of the three electrical properties: V, I, or R

$$R = \frac{V}{I}$$

Kirchhoff's Voltage Law
 $\Sigma V = 0$ (*loop*)

Kirchhoff's Current Law
 $\Sigma I = 0$ (*junction*)

Series Combination


$$R_{total} = R_1 + R_2 + \dots$$

Parallel Combination

$$\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

Calculating Circuits - Series

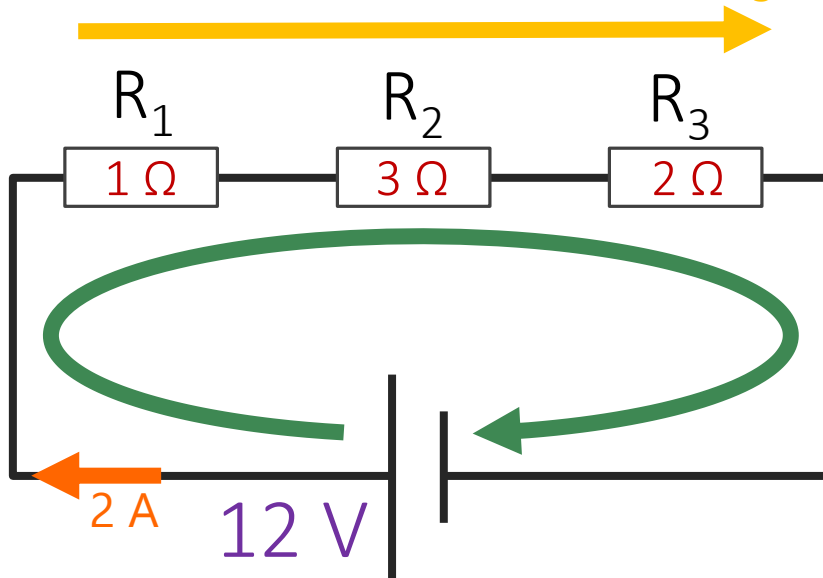No Junction: Current is the same throughout




Loop: Voltage supplied equals voltage dissipated

	V	I	R
R_1	2 V	2 A	1 Ω
R_2	6 V	2 A	3 Ω
R_3	4 V	2 A	2 Ω
Total	12 V	2 A	6 Ω

$$R_T = 1 + 3 + 2 = 6\ \Omega \quad I_T = \frac{V}{R} = \frac{12}{6} = 2\ \text{A}$$

Calculating Circuits - Parallel

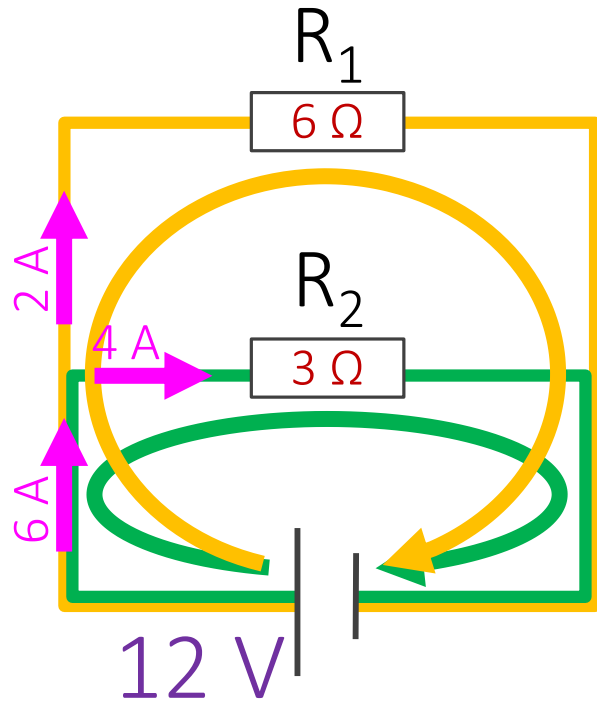

Loop: Voltage supplied equals voltage dissipated

Junction: Current in = Current out


	V	I	R
R_1	12 V	2 A	6 Ω
R_2	12 V	4 A	3 Ω
Total	12 V	6 A	2 Ω

$$R_T = (6^{-1} + 3^{-1})^{-1} = 2\ \Omega$$

$$I_T = \frac{V}{R} = \frac{12}{2} = 6\ \text{A}$$


$$I = \frac{V}{R} =$$

Patterns

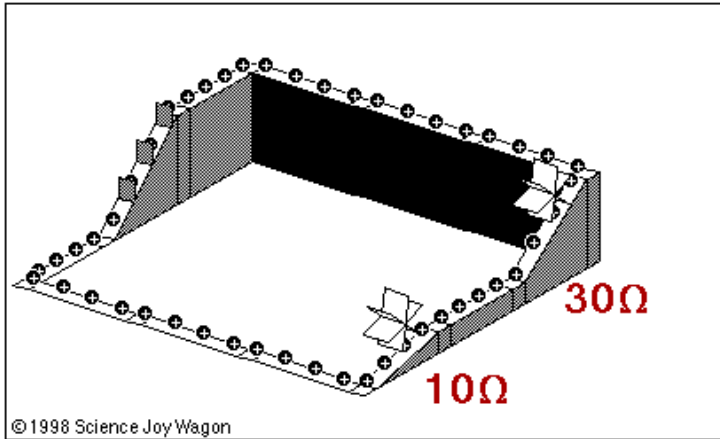

Series Circuit

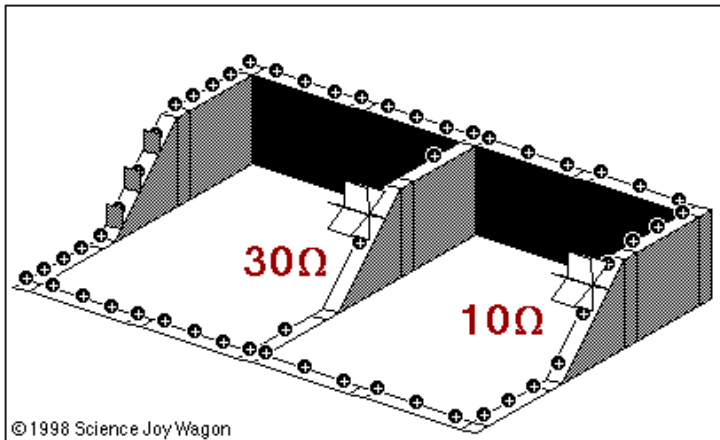- Voltage is divided between components
- Current is the same for all components



Parallel Circuit

- Voltage is the same for each branch
- Current splits at each junction

Lesson Takeaways

- ☐ I can use Kirchhoff's First Law to determine an unknown current at a junction
- ☐ I can use Kirchhoff's Second Law to determine an unknown voltage drop in a loop
- ☐ I can calculate voltage, current, and resistance for every component in a simple series or parallel circuit
- ☐ I can compare and contrast the properties for simple series and parallel circuits