

Potential Dividers


IB PHYSICS | ELECTRICITY

Types of Resistors

cell



battery

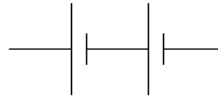


ac supply




switch



voltmeter

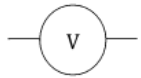


ammeter

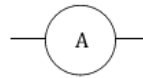


resistor




variable resistor

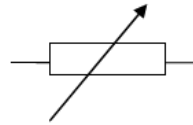

lamp

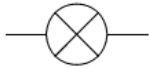


potentiometer

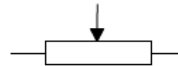

light-dependent resistor
(LDR)




thermistor

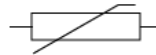

transformer





heating element

 


diode



capacitor

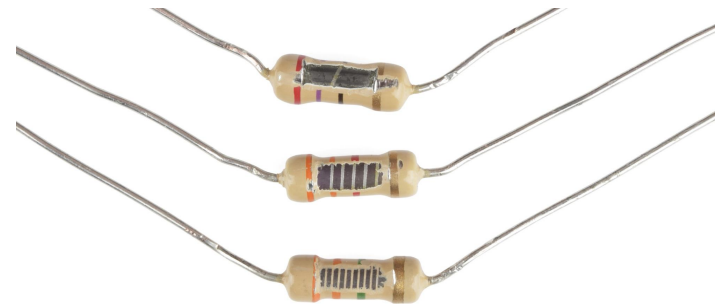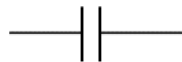


Resistor

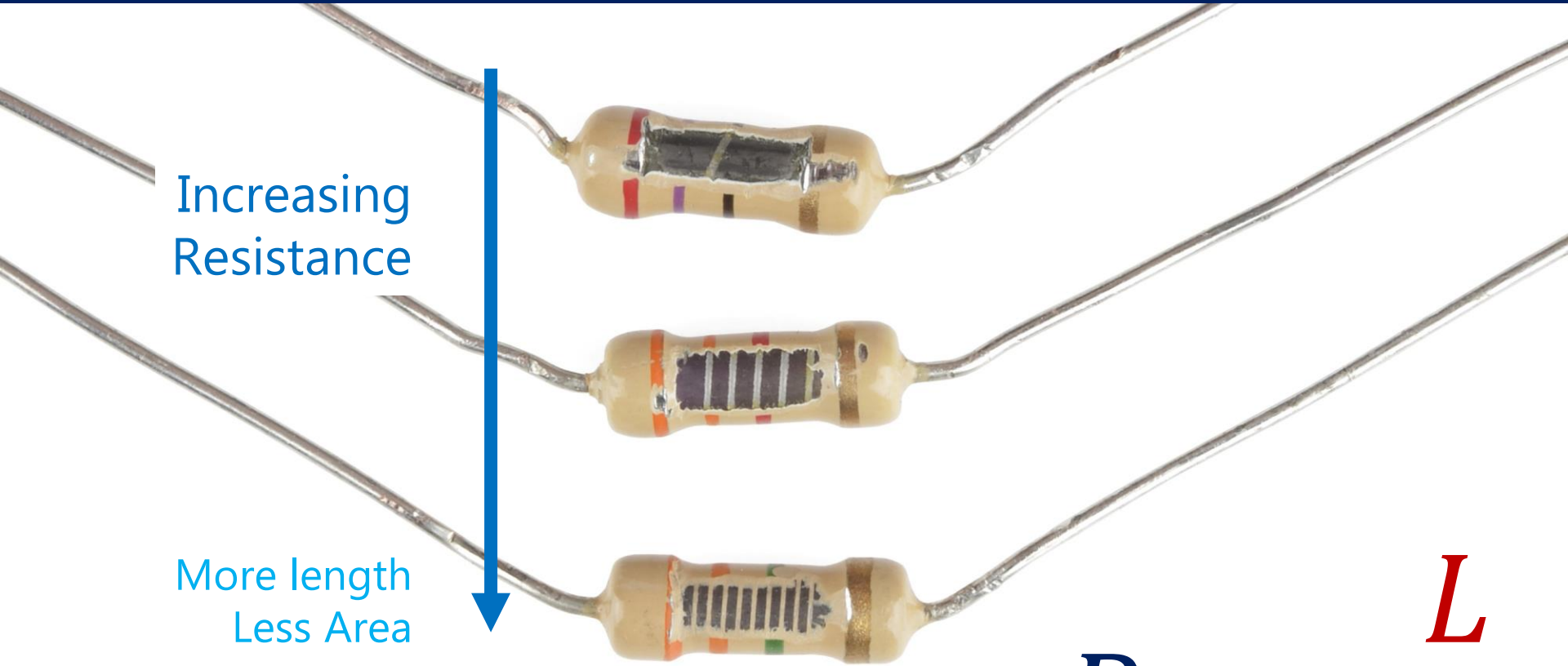


$$R = \rho \frac{L}{A}$$

Types of Resistors

cell

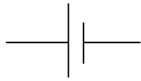

battery

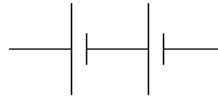


ac supply




switch



voltmeter

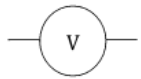


ammeter

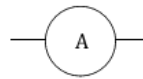

resistor



variable resistor

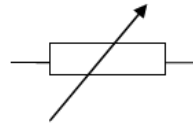

lamp




potentiometer



light-dependent resistor
(LDR)



thermistor

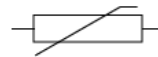

transformer





heating element



diode



capacitor

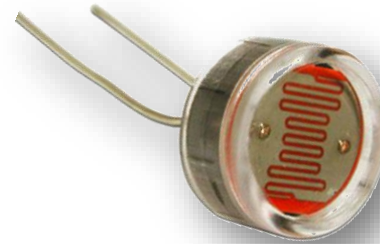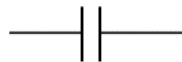

Light



Resistance

Inverse Relationship

Types of Resistors

cell		battery	
ac supply		switch	
voltmeter		ammeter	
resistor		variable resistor	
lamp		potentiometer	
light-dependent resistor (LDR)		thermistor	
transformer		heating element	
diode		capacitor	



Heat




Resistance


Inverse Relationship

Types of Resistors

cell		battery	
ac supply		switch	
voltmeter		ammeter	
resistor		variable resistor	
lamp		potentiometer	
light-dependent resistor (LDR)		thermistor	
transformer		heating element	
diode		capacitor	

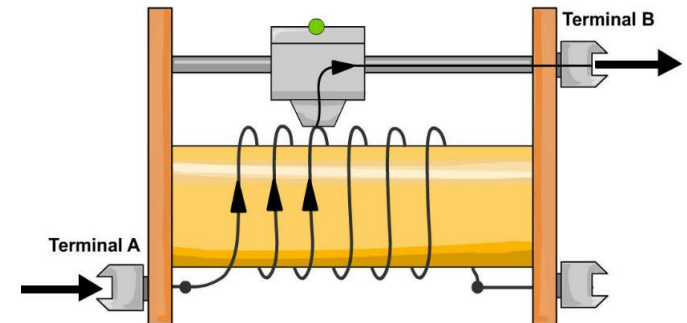


Potential Divider

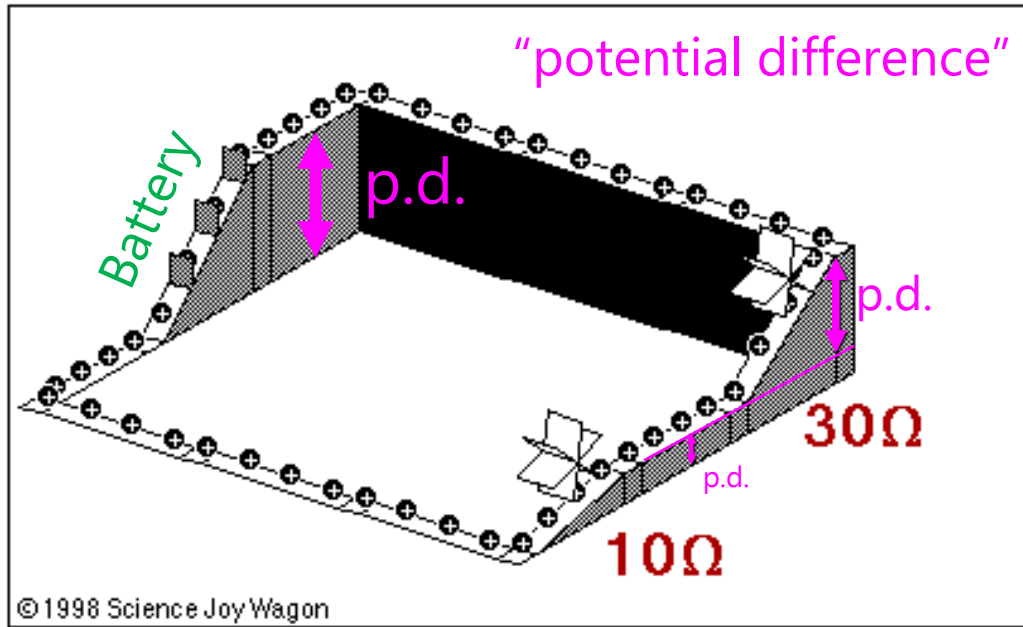


Each resistor has a “voltage drop”

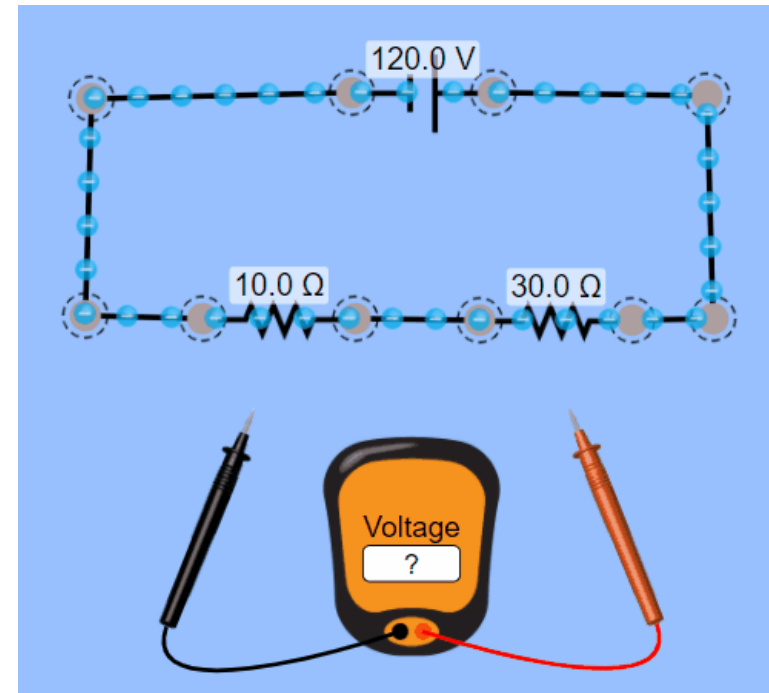The total voltage supplied by the battery is “divided” across the different resistors




Potential Divider

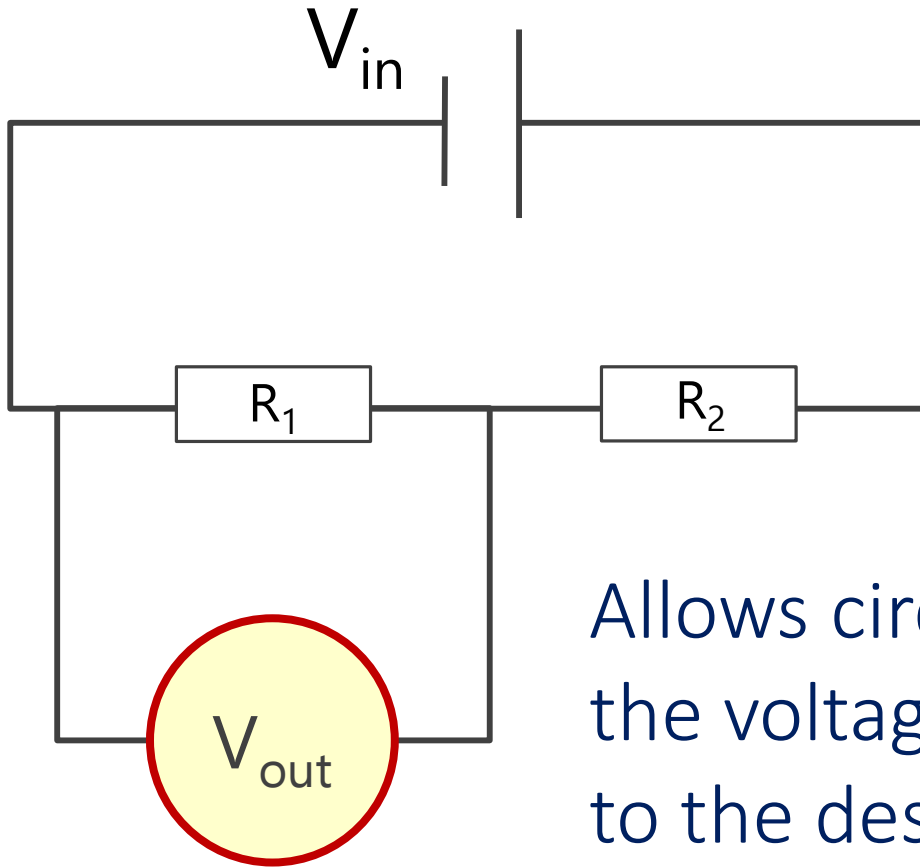

Allows circuit designers to tune the voltage that is being delivered to the desired components


Relationship between R_1 and V_{out}

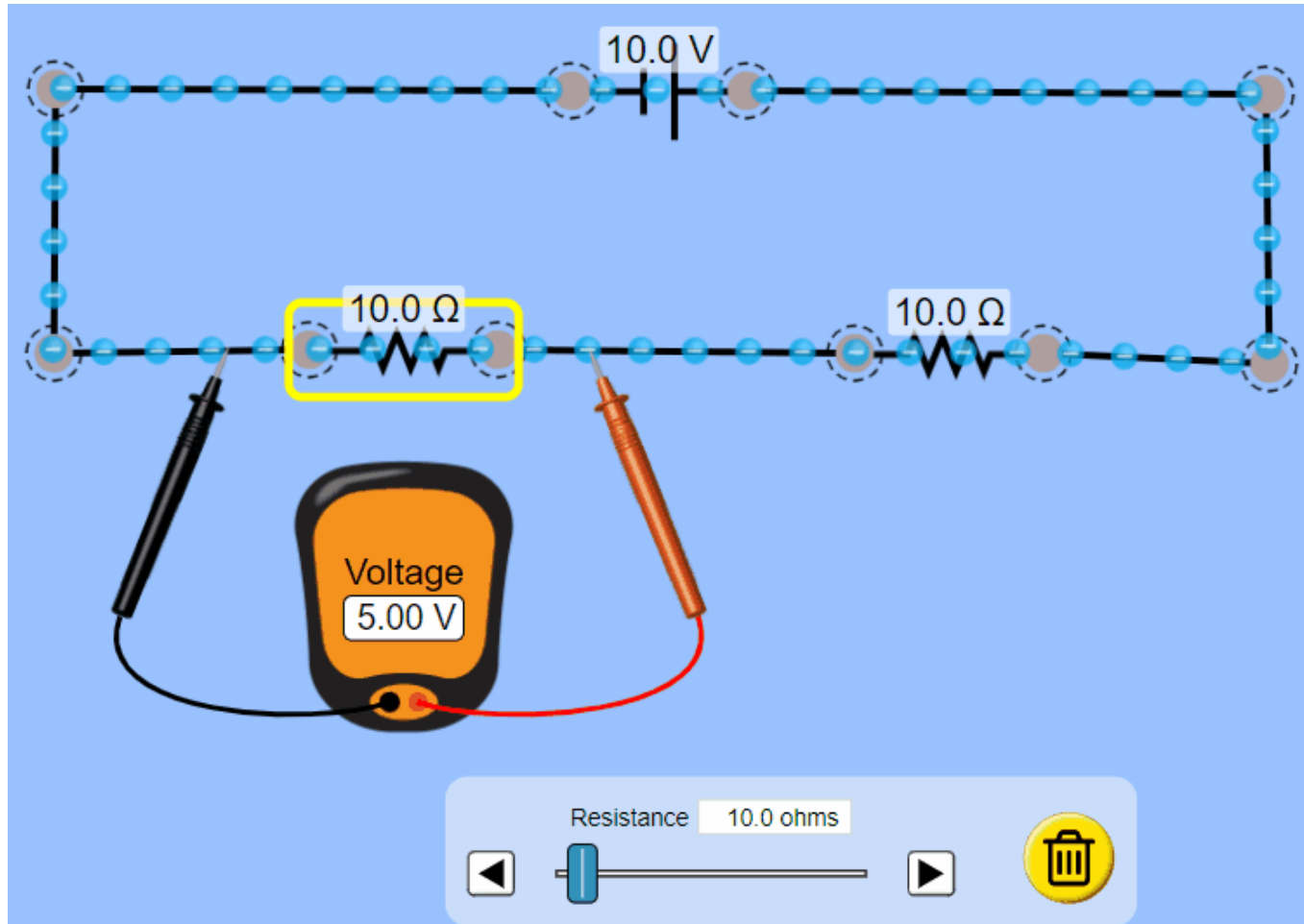

↑ R_1
↑ V_{out}

↓ R_1
↓ V_{out}


Relationship between R_2 and V_{out}

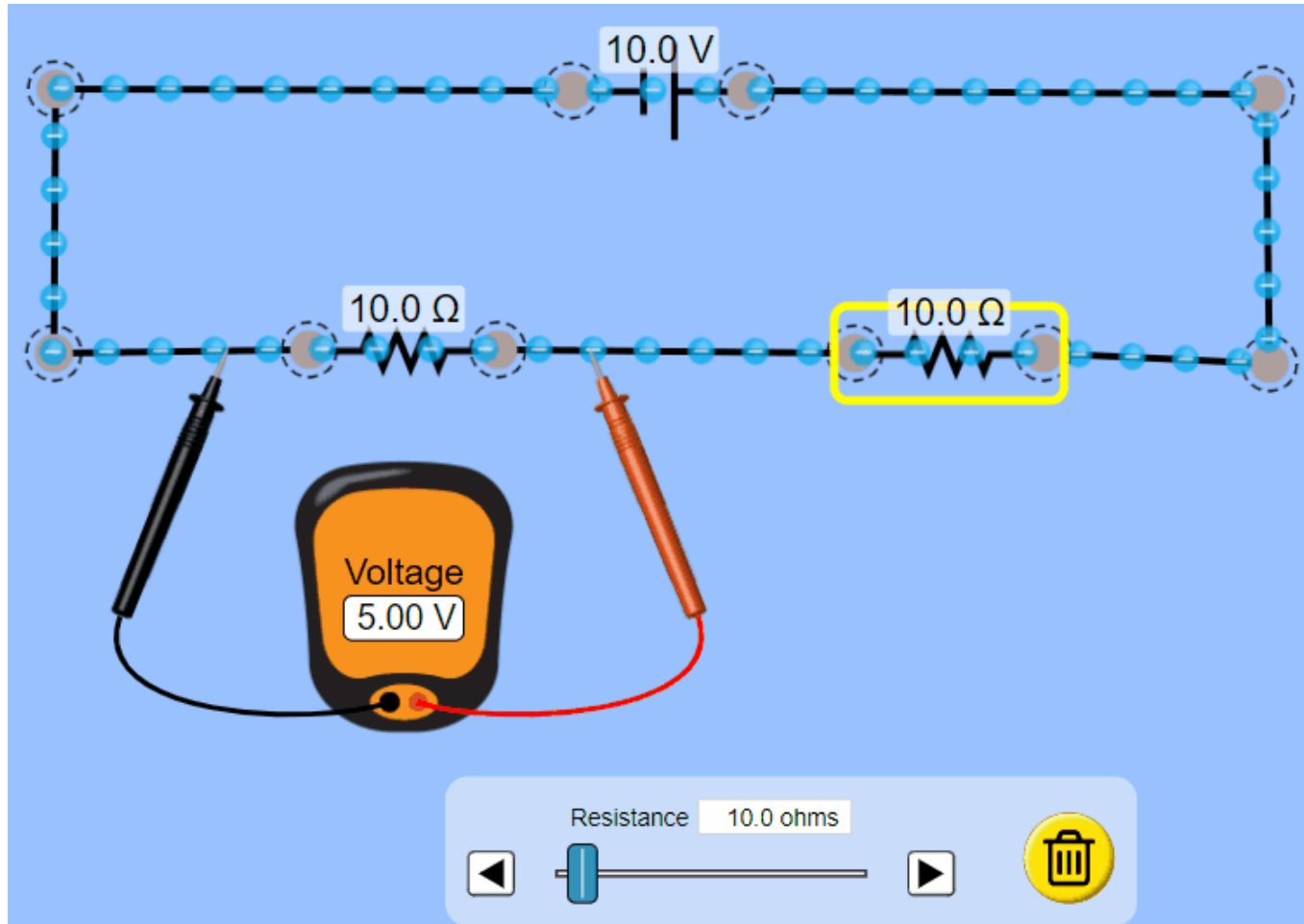

↑ R_2
↓ V_{out}

↓ R_2
↑ V_{out}

Potential Divider

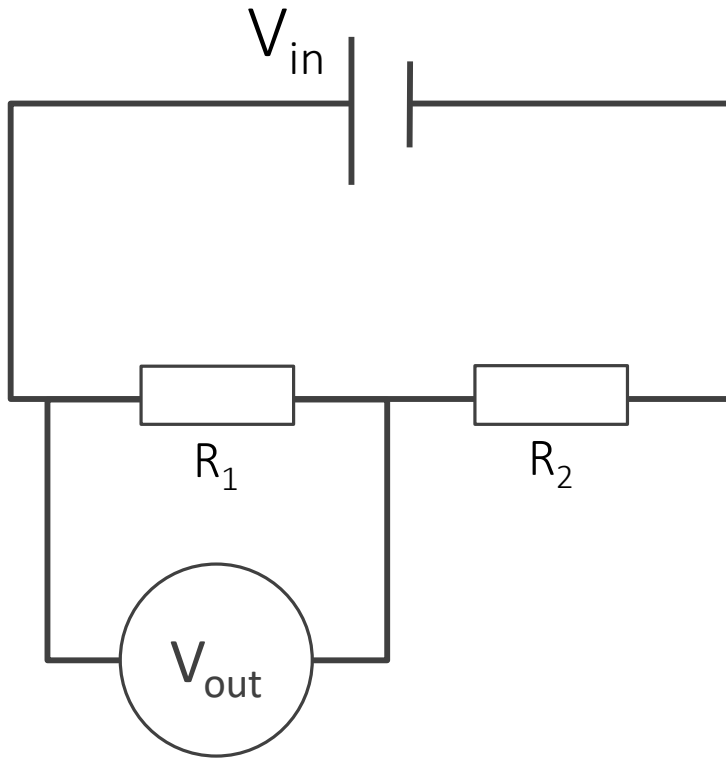

Relationship between R_1 and V ?



R_1



V_{out}



R_1



V_{out}

Relationship between R_2 and V ?



R_2



V_{out}




R_2



V_{out}

Potential Divider

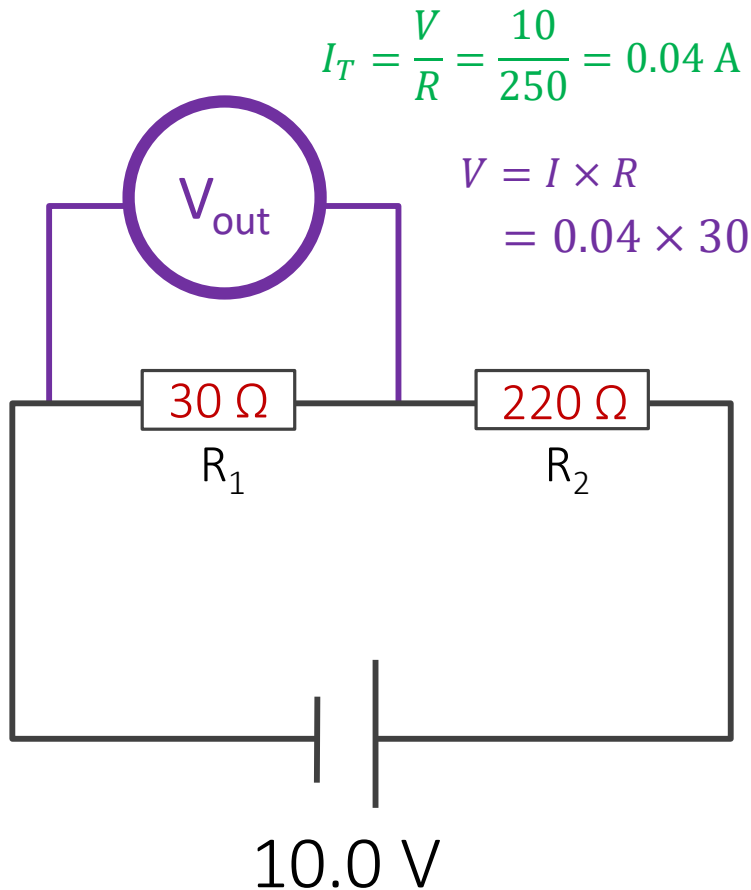



Find the Output Voltage:

	V	I	R
R_1	1.2 V	0.04 A	30 Ω
R_2		0.04 A	220 Ω
Total	10 V	0.04 A	250 Ω

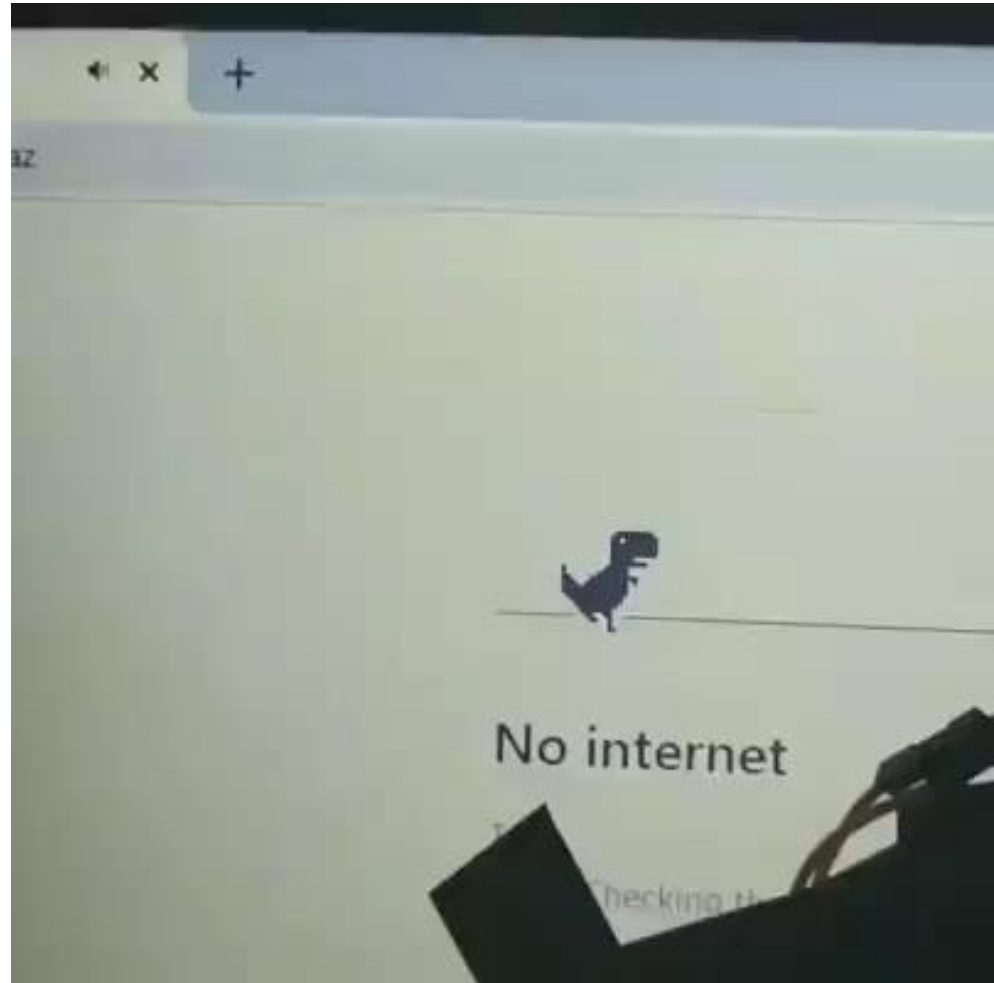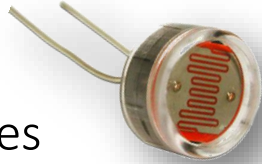
1. Calculate total resistance and current
2. Current is the same for each resistor
3. Calculate voltage across R_1

Applications of LDRs

Designed to perform function when the amount of light changes



Potential Divider | Night Light

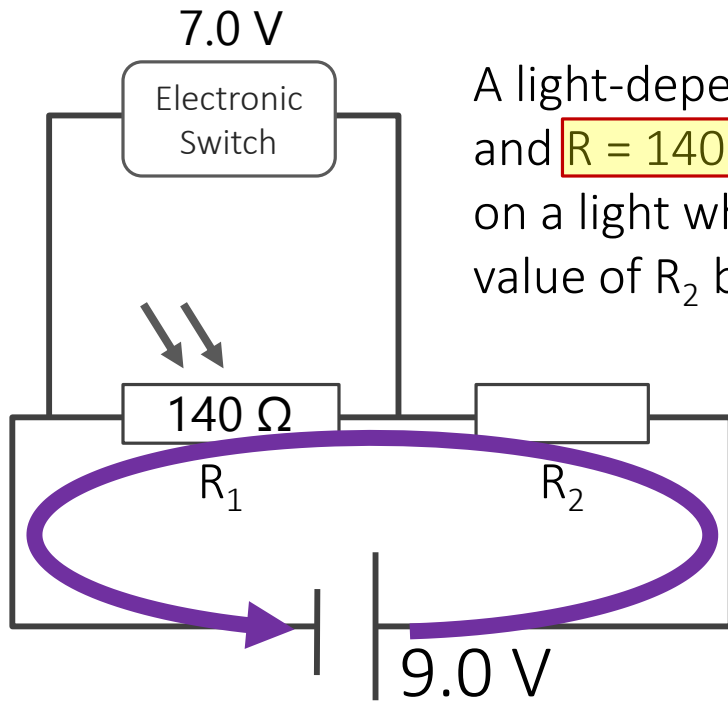


A light-dependent resistor (LDR) has $R = 8\ \Omega$ in bright light and $R = 140\ \Omega$ in low light. An electronic switch will turn on a light when its p.d. is above 7.0 V. What should the value of R_2 be?

*Night light should turn on in low light

	V	I	R
R_1	7.0 V	0.05 A	140 Ω
R_2	2.0 V	0.05 A	40 Ω
Total	9.0 V	0.05 A	

1. Calculate current through R_1
2. Current is the same throughout circuit (no current through switch)
3. Use voltage loop to find voltage across R_2
4. Calculate resistance of R_2

Potential Divider | Sprinkler System

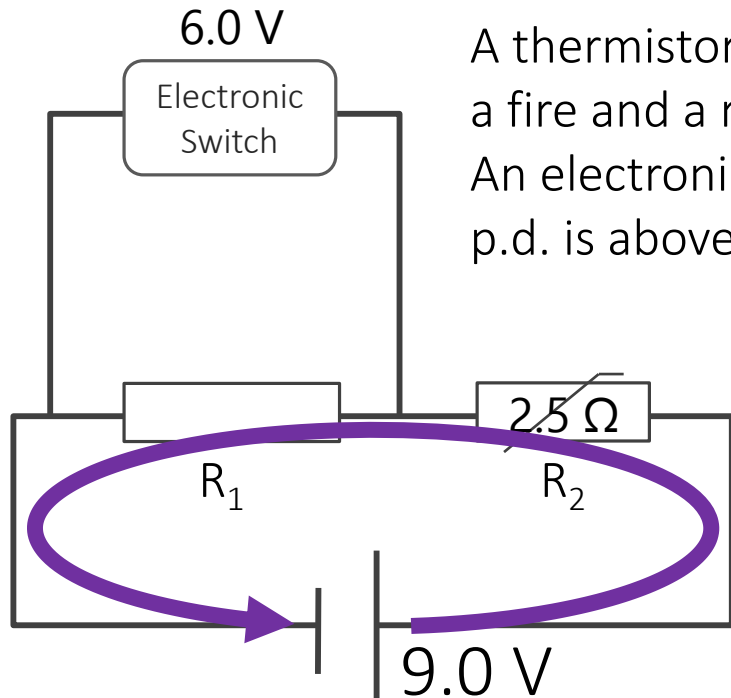

A thermistor has a resistance of 2.5Ω when it is in the heat of a fire and a resistance of 650Ω when at room temperature. An electronic switch will turn on a sprinkler system when its p.d. is above 6.0 V . What should the value of R_1 be?

*Sprinkler should activate when hot

	V	I	R
R_1	6.0 V	1.2 A	5Ω
R_2	3.0 V	1.2 A	2.5Ω
Total	9.0 V	1.2 A	

1. Use voltage loop to find voltage across R_2
2. Calculate current through R_2
3. Current is the same throughout circuit (no current through switch)
4. Calculate resistance of R_1

Lesson Takeaways

- ☐ I can identify the different circuit diagram symbols for different types of resistors
- ☐ I can describe how environmental changes can affect the resistance of LDRs and Thermistors
- ☐ I can describe how changing resistor values can affect the voltage drop in a potential divider circuit
- ☐ I can design a potential divider circuit to perform a certain task