

# Non-Ideal Meters

---

IB PHYSICS | ELECTRICITY

# The Observer Effect

*When taking any scientific measurement, there is always the possibility that the act of taking the measurement will change what is being measured*




# The Observer Effect


When we measure **voltage** or **current** in a circuit, we want to make sure to minimize an effect that our tool has on the circuit so that we get the most accurate results



Voltmeter

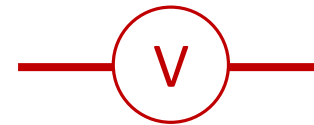


Ammeter

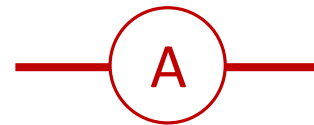
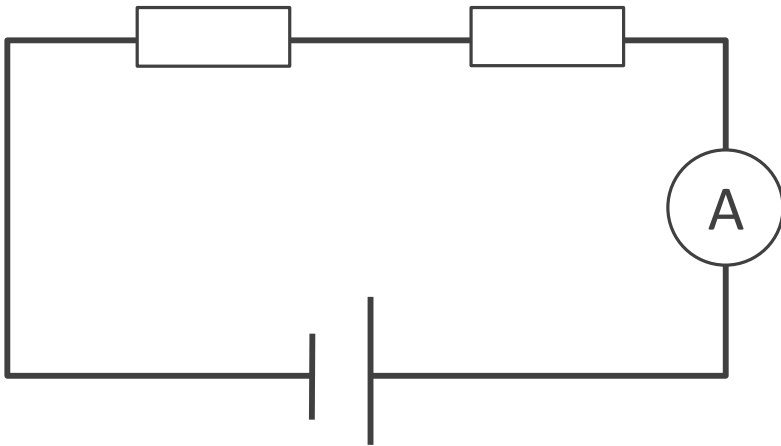
# Ammeter

Hooked up in series with the component being measured




**Ideal Ammeter:**

$$[R = 0 \, \Omega]$$
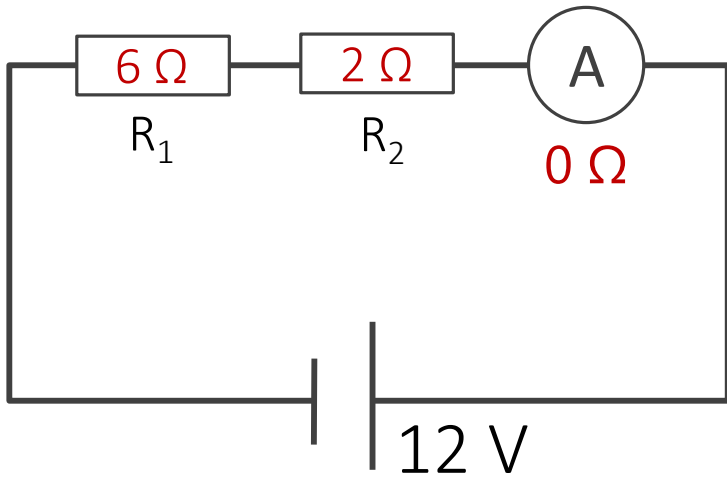
# Measuring the Current

What is the reading for the current flowing through this ideal ammeter?




$$R_T = 8\ \Omega$$

$$I = \frac{V}{R} = \frac{12}{8} = 1.5\ \text{A}$$

The ammeter has no effect on the current that it's measuring
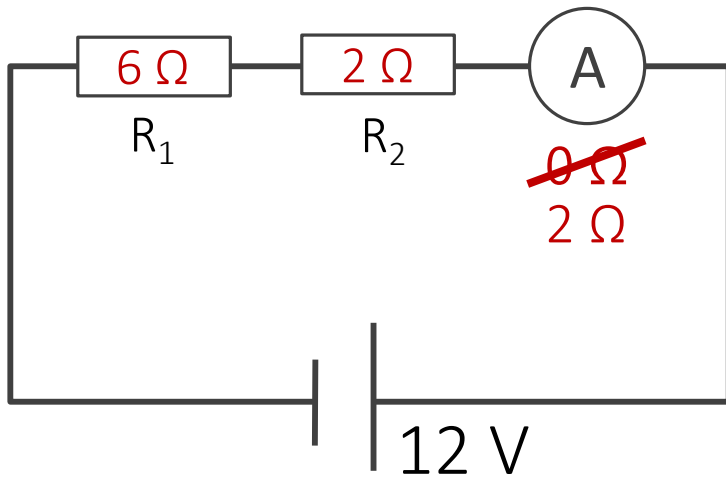
# What if Ammeter isn't ideal?

What is the reading for the current flowing through this ~~ideal~~<sup>2  $\Omega$</sup>  ammeter?




$$R_T = \overset{10\ \Omega}{\cancel{8\ \Omega}}$$

$$I = \frac{V}{R} = \frac{12}{\underset{10}{\cancel{8}}} = \overset{1.2\ \text{A}}{\cancel{1.5\ \text{A}}}$$

The non-ideal ammeter's resistance slows down the current that it's measuring
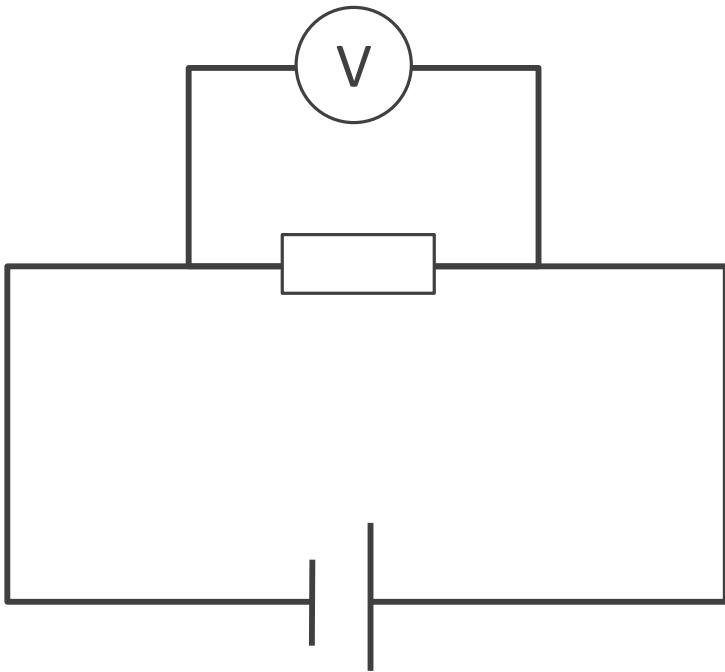
# Voltmeter


Hooked up in parallel with the component being measured



**Ideal Voltmeter:**

$$[R = \infty \Omega]$$

# Measuring the Voltage

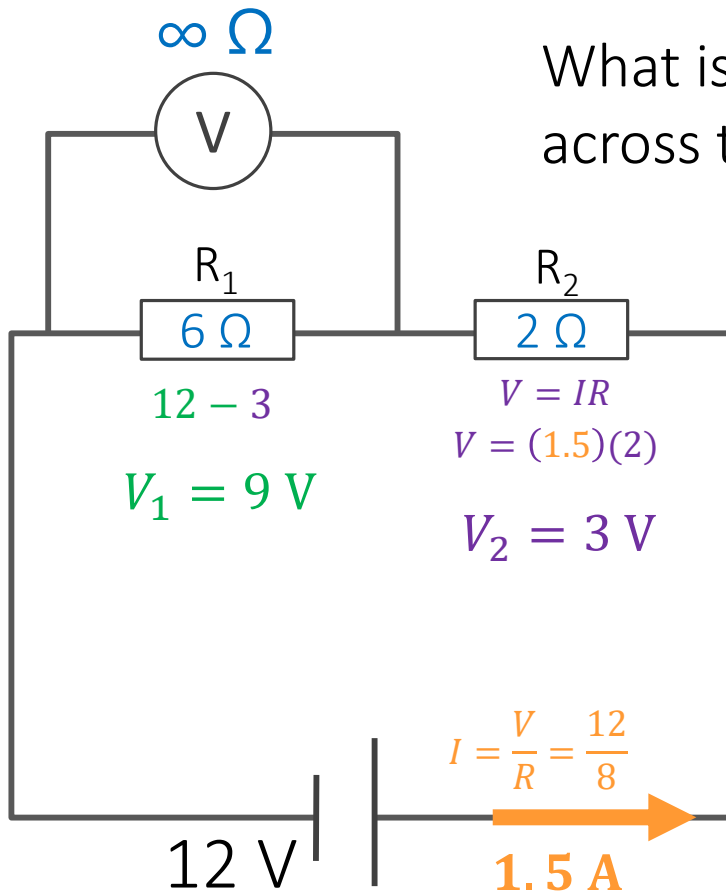

What is the reading for the ideal voltmeter across the resistor  $R_1$ ?


$$R_T = \frac{1}{\frac{1}{6} + \frac{1}{\infty}} + 2$$

0

$$R_T = 6 + 2 = 8\ \Omega$$



# Measuring the Voltage

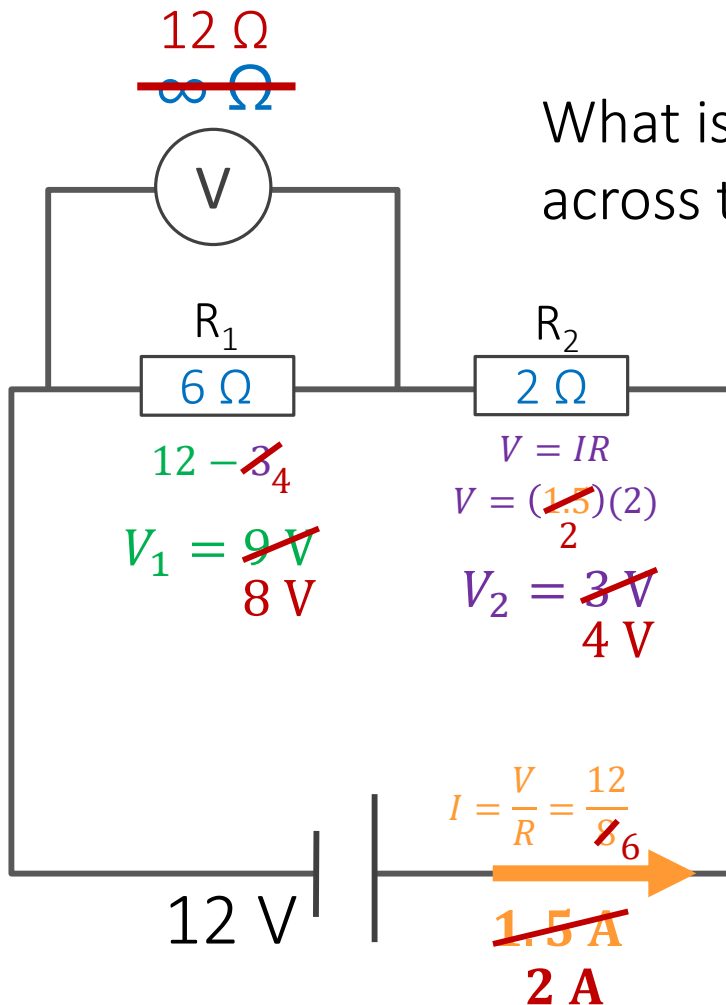

What is the reading for the ~~ideal~~ <sup>12 Ω</sup> voltmeter across the resistor  $R_1$ ?

$$R_T = \frac{1}{\frac{1}{6} + \frac{1}{\infty}} + 2$$

$$R_T = \frac{6}{4} + 2 = \frac{8}{6} \Omega$$


# Try This

Calculate the resistance of this non-ideal meter:

Ammeter  
Reading

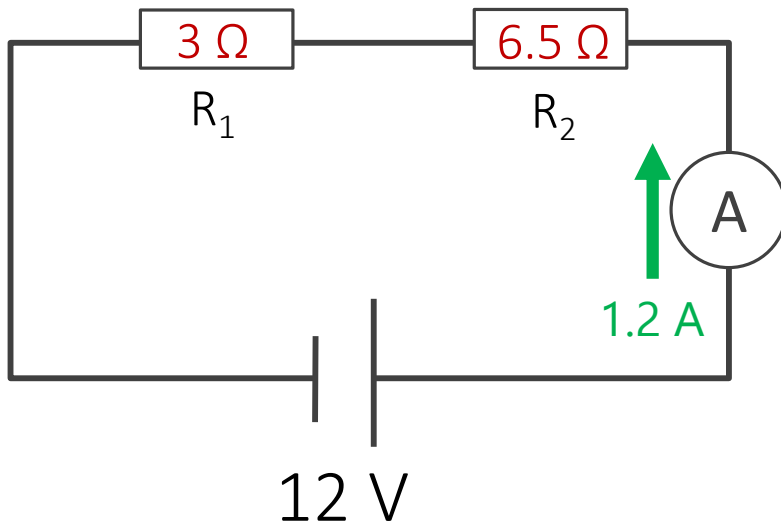1.2 A

- Current is the same for all components
- Calculate total resistance from voltage and current
- Calculate ammeter resistance



$$R = \frac{V}{I} = \frac{12}{1.2} = 10\ \Omega$$

$$R_T = 10\ \Omega = 3 + 6.5 + A$$

$$A = 0.5\ \Omega$$


# Try This

Calculate the resistance of this non-ideal meter:

Voltmeter  
Reading

7 V

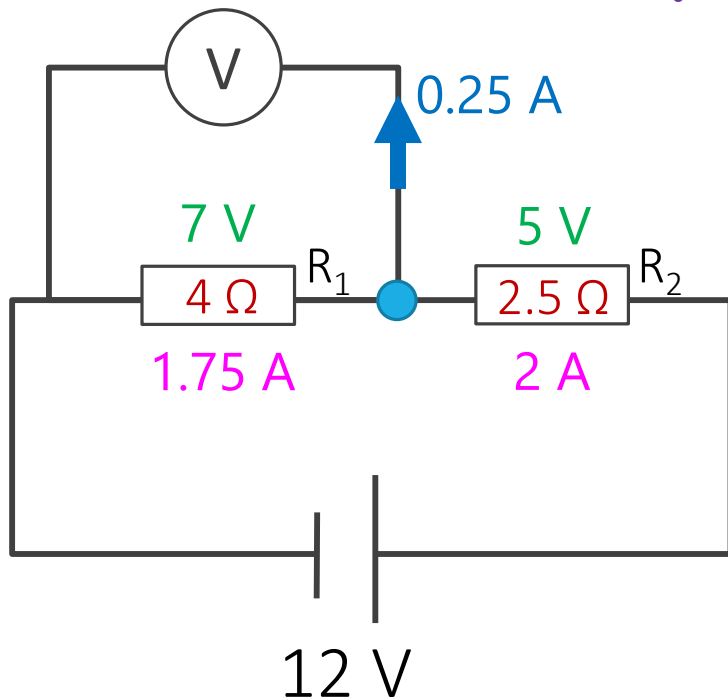
- Use voltage loops to calculate voltage for  $R_1$  and  $R_2$
- Calculate current for  $R_1$  and  $R_2$
- Use current junction to find current through meter
- Calculate resistance of voltmeter



$$I = \frac{V}{R}$$

$$R = \frac{V}{I} = \frac{7}{0.25}$$

$$R = 28 \Omega$$

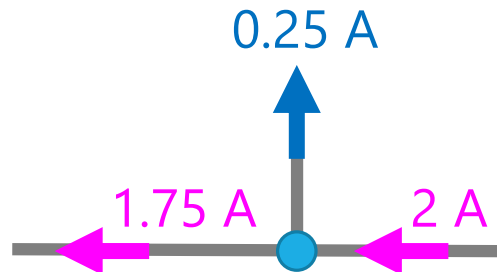

# Lesson Takeaways

- ☐ I can connect a meter to measure current or voltage
- ☐ I can describe the conditions required for an ideal ammeter or voltmeter
- ☐ I can calculate for a situation when the meter isn't ideal