

Batteries

IB PHYSICS | ELECTRICITY

Batteries



Primary Cells

One time use



Secondary Cells

Rechargeable

Battery Shape	Chemistry	Nominal Voltage	Rechargeable?
AA, AAA, C, and D	Alkaline or Zinc-carbon	1.5V	No
9V	Alkaline or Zinc-carbon	9V	No
Coin cell	Lithium	3V	No
Silver Flat Pack	Lithium Polymer (LiPo)	3.7V	Yes
AA, AAA, C, D (Rechargeable)	NiMH or NiCd	1.2V	Yes
Car battery	Six-cell lead-acid	12.6V	Yes

Recharging?

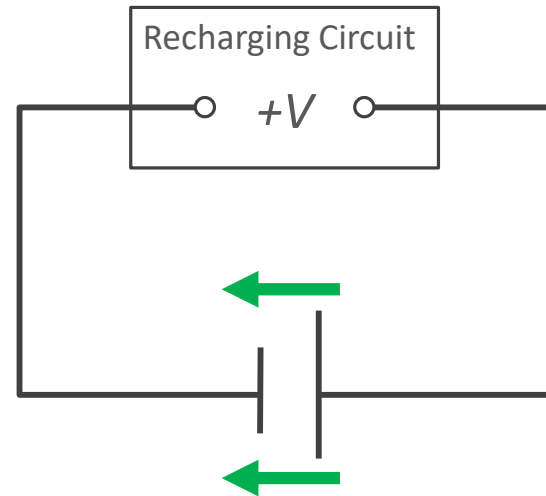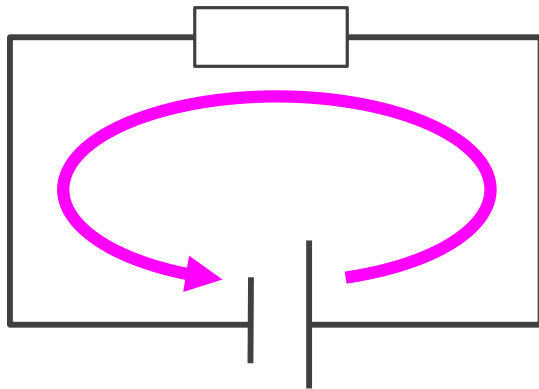Some batteries can reverse the chemical reaction that produces the potential difference by passing a current through the battery in the opposite direction as it would normally travel




Batteries | emf

We've been describing batteries so far as the voltage that they provide to the circuit, but that's not the whole story...

Electromotive Force (emf)

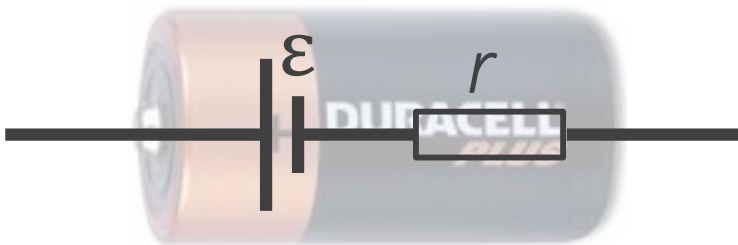The total energy transferred in the source per unit charge passing through it



Symbol


\mathcal{E}

Unit

Volts [V]

Batteries | Internal Resistance

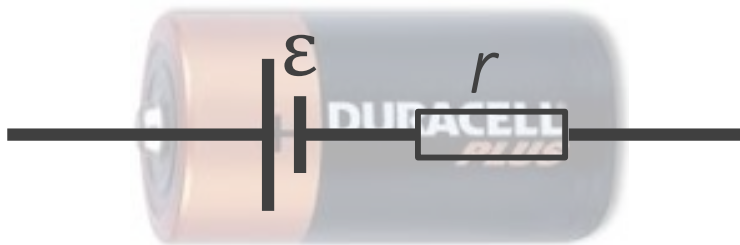All batteries have some amount of internal resistance



Symbol
r

Unit
Ohms [Ω]


Batteries | emf

What is the emf for a battery shown below?

$$R_T = 7 + 3 + 0.5 = 10.5 \, \Omega$$

$$\varepsilon = IR_T = (1.2)(10.5)$$

$$\varepsilon = 12.6 \, \text{V}$$

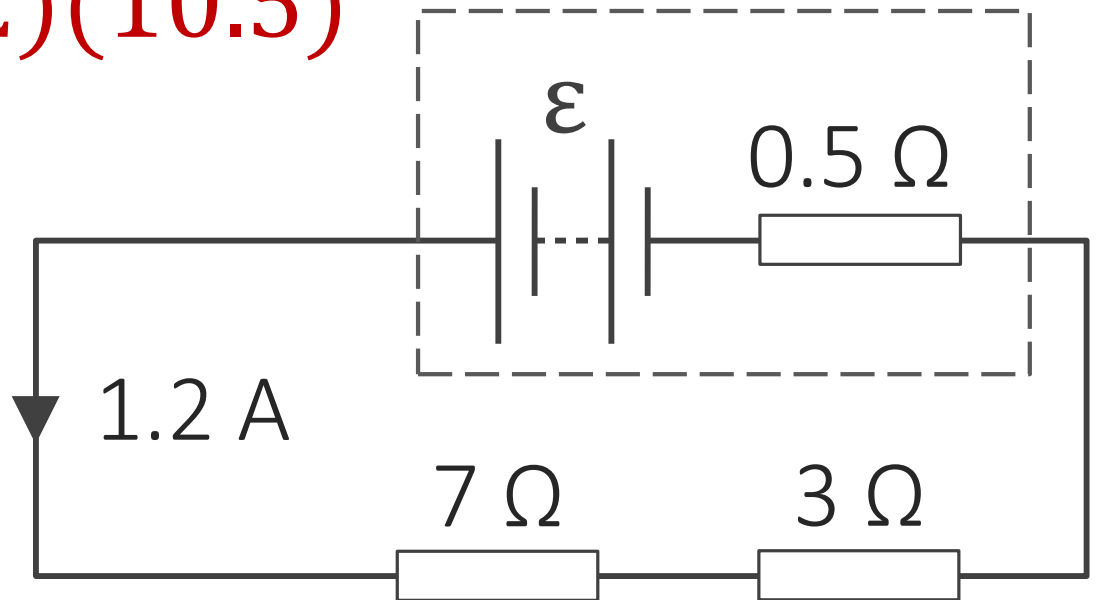

IB Physics Data Booklet

Sub-topic 5.1 – Electric fields

$$I = \frac{\Delta q}{\Delta t}$$

$$F = k \frac{q_1 q_2}{r^2}$$

$$k = \frac{1}{4\pi\epsilon_0}$$

$$V = \frac{W}{q}$$

$$E = \frac{F}{q}$$

$$I = nAvq$$

Sub-topic 5.2 – Heating effect of electric currents

Kirchhoff's circuit laws:

$$\Sigma V = 0 \text{ (loop)}$$

$$\Sigma I = 0 \text{ (junction)}$$

$$R = \frac{V}{I}$$

$$P = VI = I^2 R = \frac{V^2}{R}$$

$$R_{\text{total}} = R_1 + R_2 + \dots$$

$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$\rho = \frac{RA}{L}$$

Sub-topic 5.3 – Electric cells

$$\mathcal{E} = I(R + r)$$

Essentially the same as $V = IR$

Sub-topic 5.4 – Magnetic effects of electric currents

$$F = qvB \sin \theta$$

$$F = BIL \sin \theta$$


Batteries | emf

What is the emf for a battery shown below?

$$R_T = \overset{\text{R}}{7 + 3} + \overset{\text{r}}{0.5} = 10.5 \, \Omega$$

$$\varepsilon = IR_T = (1.2)(10.5)$$

$$\varepsilon = 12.6 \, \text{V}$$

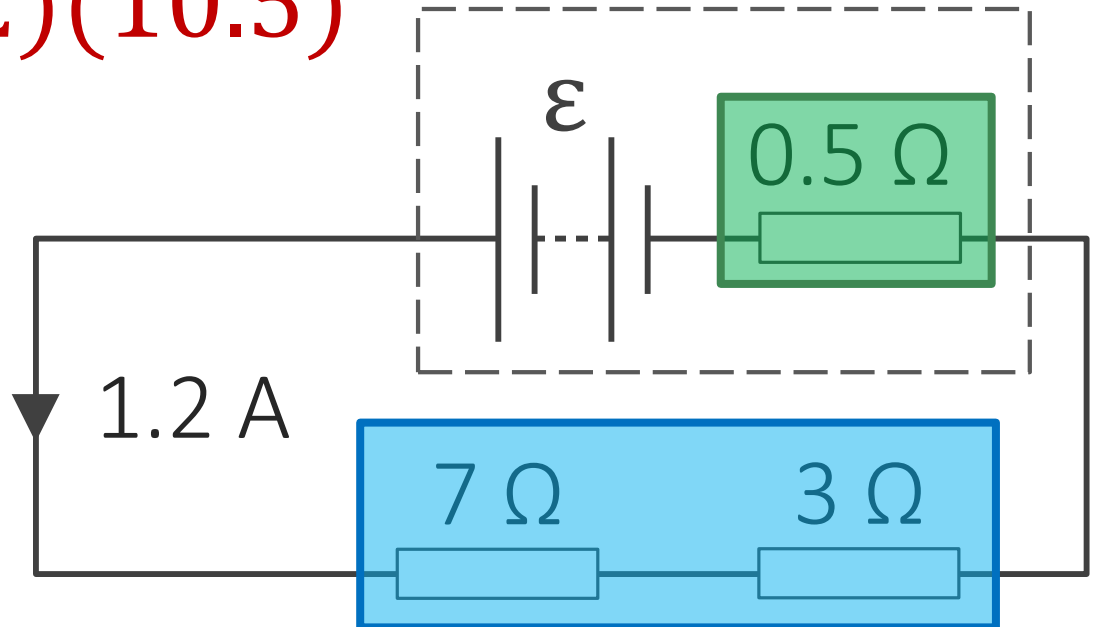

Batteries | Terminal Voltage


What is the terminal voltage for a battery shown below?

$$V_1 = IR = (1.2)(7) = 8.4 \text{ V}$$

$$V_2 = IR = (1.2)(3) = 3.6 \text{ V}$$

$$V_T = 8.4 \text{ V} + 3.6 \text{ V}$$

$$V_T = 12 \text{ V}$$

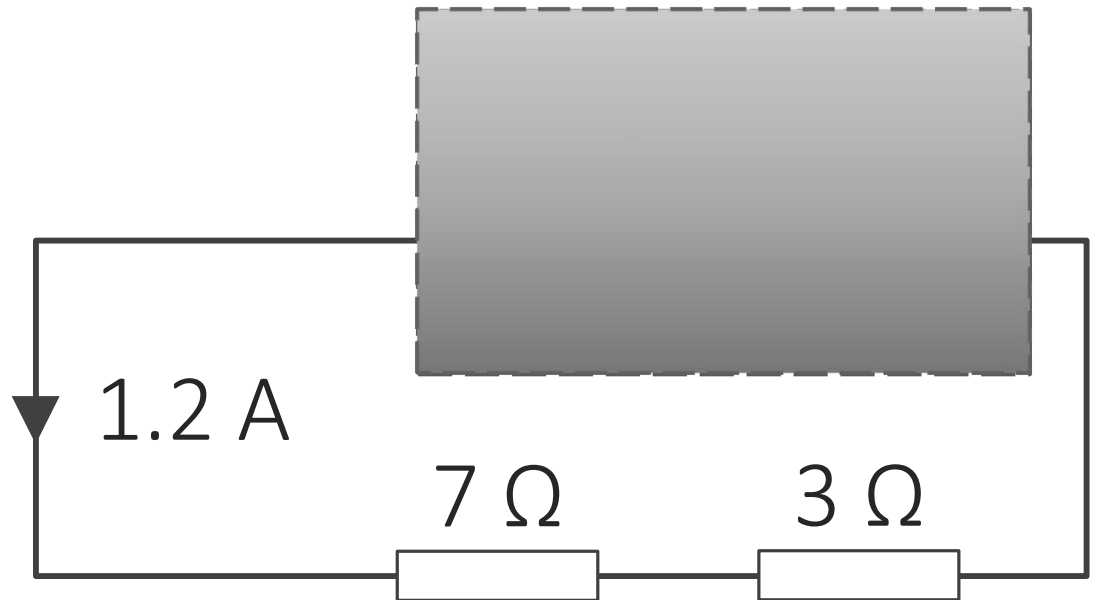


Batteries | Internal Resistance

What is the internal resistance of this battery as shown below?

$$\varepsilon = I(R + r)$$

$$9 = 3(2.5 + r)$$

$$r = 0.5 \, \Omega$$

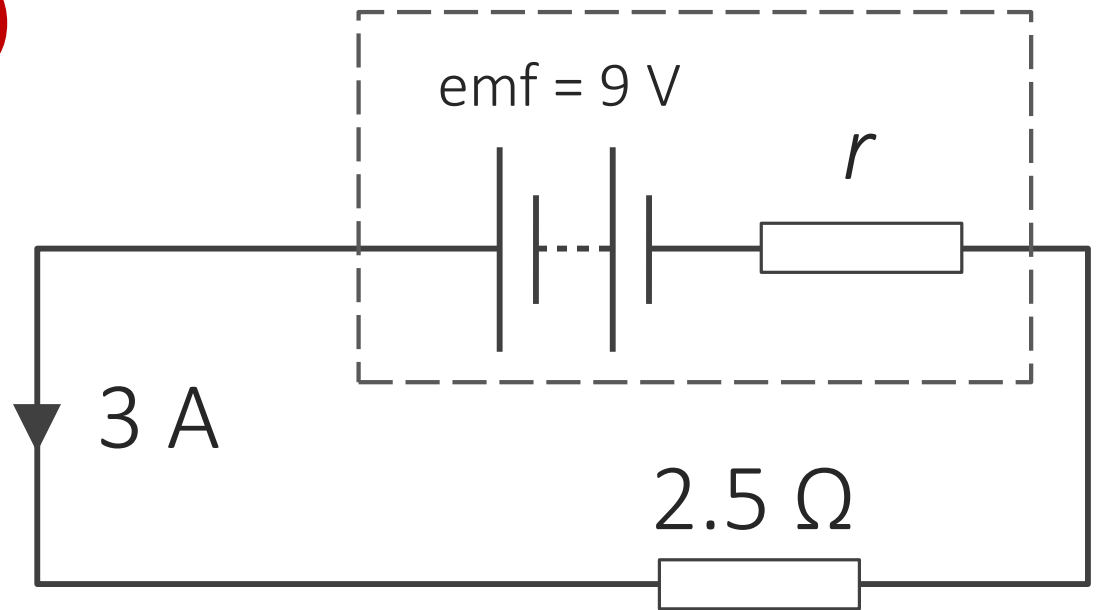

Graphing Internal Resistance


$$\varepsilon = I(R + r)$$

$$\varepsilon = IR + Ir$$

$$V = IR$$

$$\varepsilon = V + Ir$$

$$V = \varepsilon - Ir$$

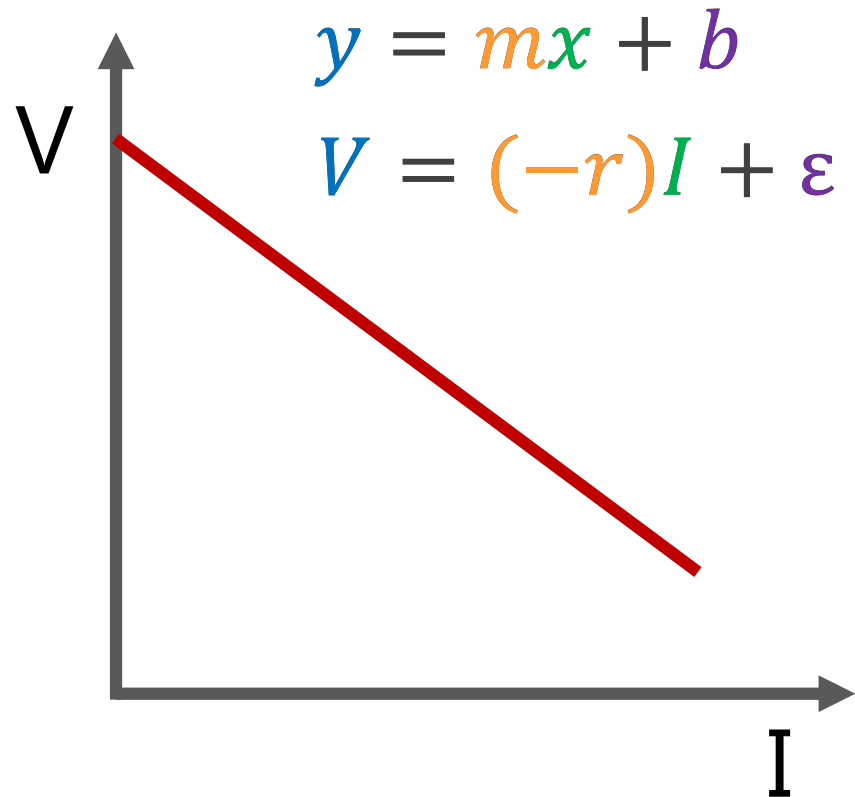

Lesson Takeaways

- ☐ I can describe the difference between primary and secondary cells
- ☐ I can define the electromotive force and describe how it is different than the battery's terminal voltage
- ☐ I can solve for a circuit that includes a battery with internal resistance
- ☐ I can describe how